

---

# **Computer Logic Design Fundamentals**

## **Chapter 2 – Combinational Logic Circuits**

### **Part 1 – Gate Circuits and Boolean Equations**

Prof. Yueming Wang

[ymingwang@zju.edu.cn](mailto:ymingwang@zju.edu.cn)

College of Computer Science and Technology,  
Zhejiang University

# Overview

---

- **Part 1 – Gate Circuits and Boolean Equations**
  - **Binary Logic and Gates**
  - **Boolean Algebra**
  - **Standard Forms**
- **Part 2 – Circuit Optimization**
  - **Two-Level Optimization**
  - **Map Manipulation**
  - **Practical Optimization (Espresso)**
  - **Multi-Level Circuit Optimization**
- **Part 3 – Additional Gates and Circuits**
  - **Other Gate Types**
  - **Exclusive-OR Operator and Gates**
  - **High-Impedance Outputs**
  - **Propagation Delay**

# Binary Logic and Gates

---

- Binary variables take on one of two values.
- Logical operators operate on binary values and binary variables.
- Basic logical operators are the logic functions AND, OR and NOT.
- Logic gates implement logic functions.
- Boolean Algebra: a useful mathematical system for specifying and transforming logic functions.
- We study Boolean algebra as a foundation for designing and analyzing digital systems!

# Binary Variables

---

- **Recall that the two binary values have different names:**
  - **True/False**
  - **On/Off**
  - **Yes/No**
  - **1/0**
- **We use 1 and 0 to denote the two values.**
- **Variable identifier examples:**
  - **A, B, y, z, or  $X_1$  for now**
  - **RESET, START\_IT, or ADD1 later**

# Logical Operations

---

- **The three basic logical operations are:**
  - **AND**
  - **OR**
  - **NOT**
- **AND is denoted by a dot ( $\cdot$ ).**
- **OR is denoted by a plus ( $+$ ).**
- **NOT is denoted by an overbar ( $\bar{\phantom{x}}$ ), a single quote mark ( $'$ ) after, or ( $\sim$ ) before the variable.**

# Notation Examples

---

## ■ Examples:

- $Y = A \times B$  is read “Y is equal to A AND B.”
- $z = x + y$  is read “z is equal to x OR y.”
- $X = \bar{A}$  is read “X is equal to NOT A.”

## ■ Note: The statement:

$1 + 1 = 2$  (read “one plus one equals two”)

is not the same as

$1 + 1 = 1$  (read “1 or 1 equals 1”).

# Operator Definitions

---

- Operations are defined on the values "0" and "1" for each operator:

**AND**

$$0 \cdot 0 = 0$$

$$0 \cdot 1 = 0$$

$$1 \cdot 0 = 0$$

$$1 \cdot 1 = 1$$

**OR**

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 1$$

**NOT**

$$\bar{0} = 1$$

$$\bar{1} = 0$$

# Truth Tables

- *Truth table* – a tabular listing of the values of a function for all possible combinations of values on its arguments
- Example: Truth tables for the basic logic operations:

AND		
X	Y	$Z = X \cdot Y$
0	0	0
0	1	0
1	0	0
1	1	1

OR		
X	Y	$Z = X + Y$
0	0	0
0	1	1
1	0	1
1	1	1

NOT	
X	$Z = \overline{X}$
0	1
1	0




# Logic Function Implementation


## ■ Using Switches

- For inputs:
  - logic 1 is switch closed
  - logic 0 is switch open
- For outputs:
  - logic 1 is light on
  - logic 0 is light off.
- NOT uses a switch such that:
  - logic 1 is switch open
  - logic 0 is switch closed


Switches in parallel => OR

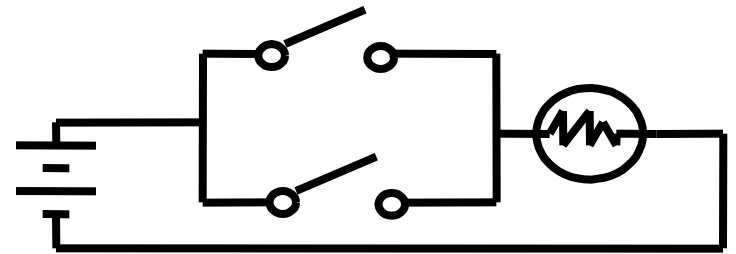

Switches in series => AND

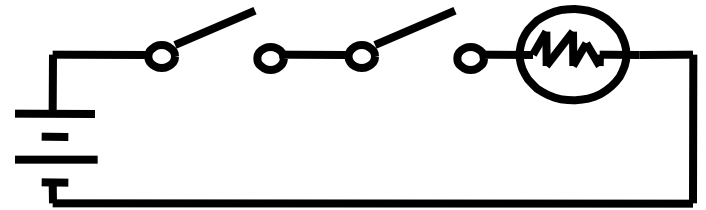


Normally-closed switch => NOT

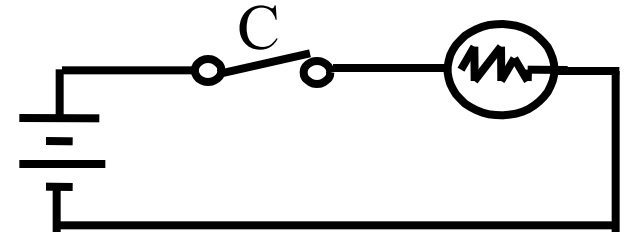

# Logic Function Implementation (Continued)

- **Example: Logic Using Switches**

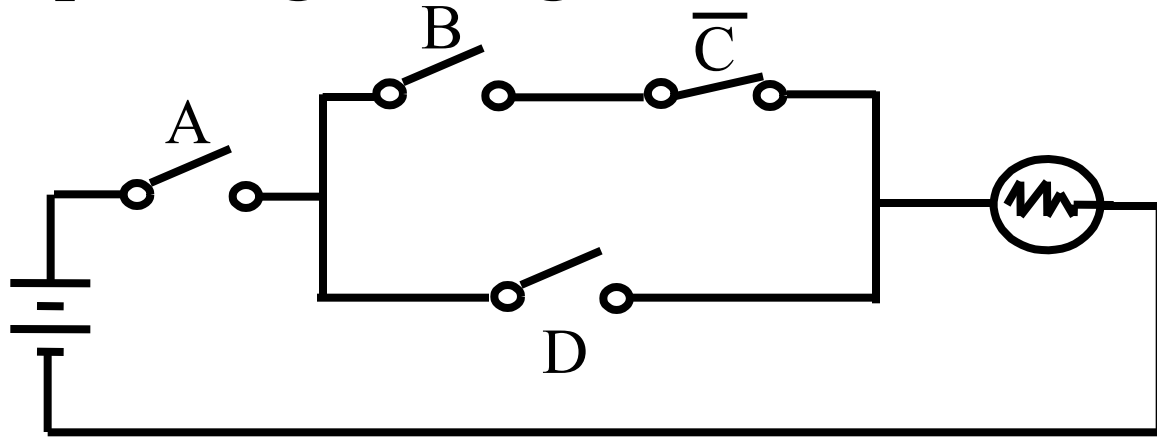

- **Light is on ( $L = 1$ ) for**


$$L(A, B, C, D) =$$

**and off ( $L = 0$ ), otherwise.**

- **Useful model for relay circuits and for CMOS gate circuits, the foundation of current digital logic technology**

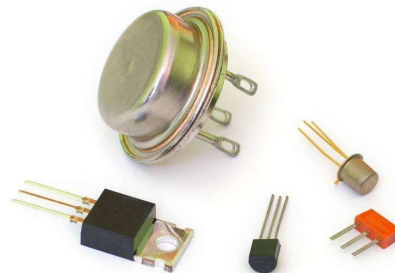
# Logic Gates

- In the earliest computers, switches were opened and closed by magnetic fields produced by energizing coils in *relays*. The switches in turn opened and closed the current paths.
- Later, *vacuum tubes* that open and close current paths electronically replaced relays.
- Today, *transistors* are used as electronic switches that open and close current paths.



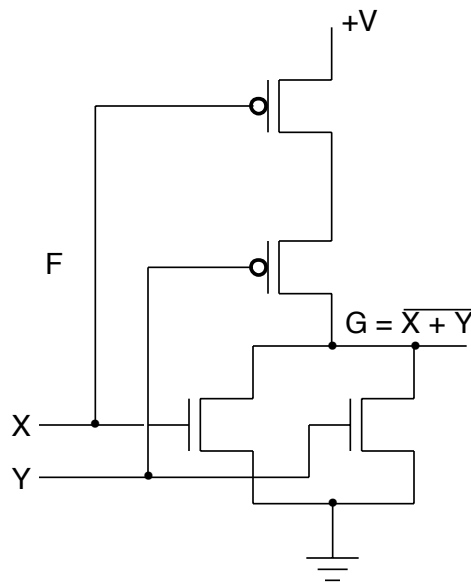
# Logic Gates (Continued)


- Implementation of logic gates with transistors (See Reading Supplement – CMOS Circuits)



(a) NOR

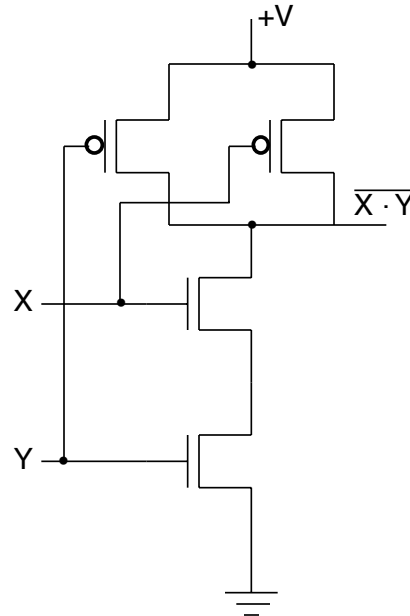

(b) NAND

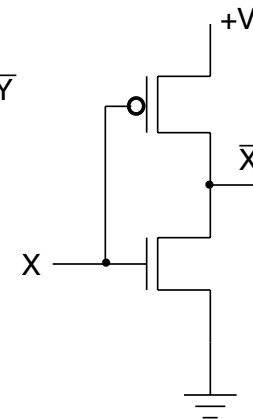


(c) NOT

- Transistor or tube implementations of logic functions are called logic gates or just gates
- Transistor gate circuits can be modeled by switch circuits


# Logic Gate Symbols and Behavior

- Logic gates have special symbols:

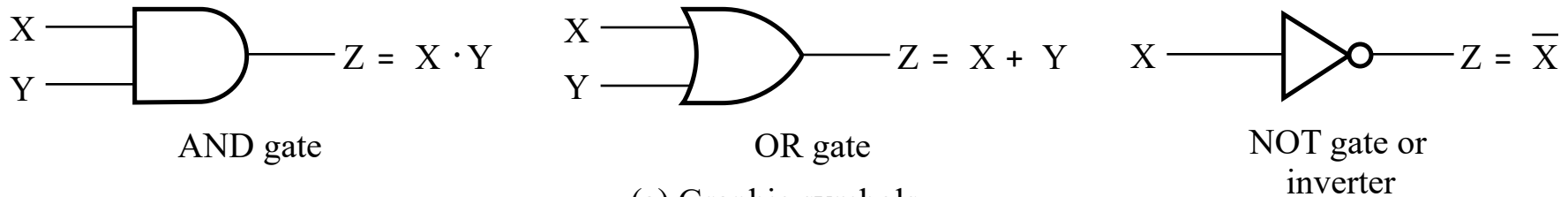

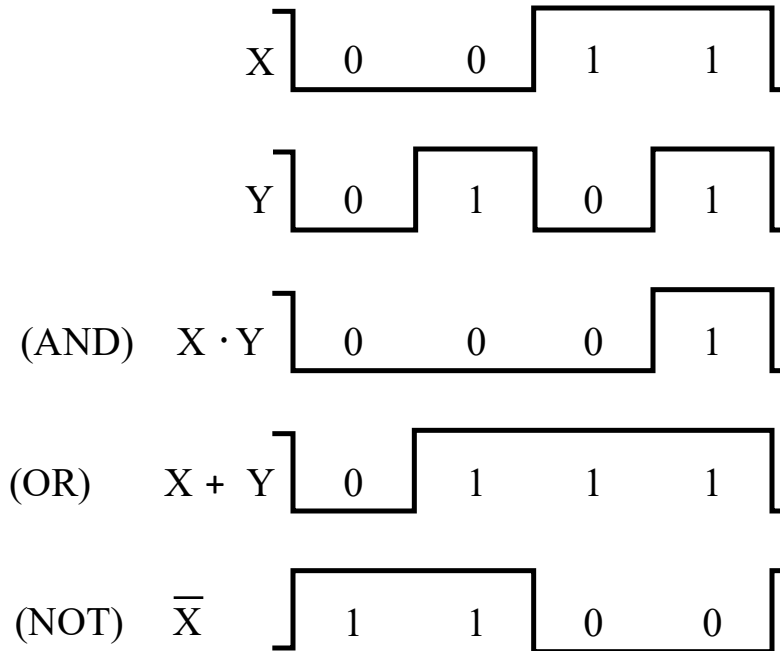(a) Graphic symbols


- And waveform behavior in time as follows:



(b) Timing diagram
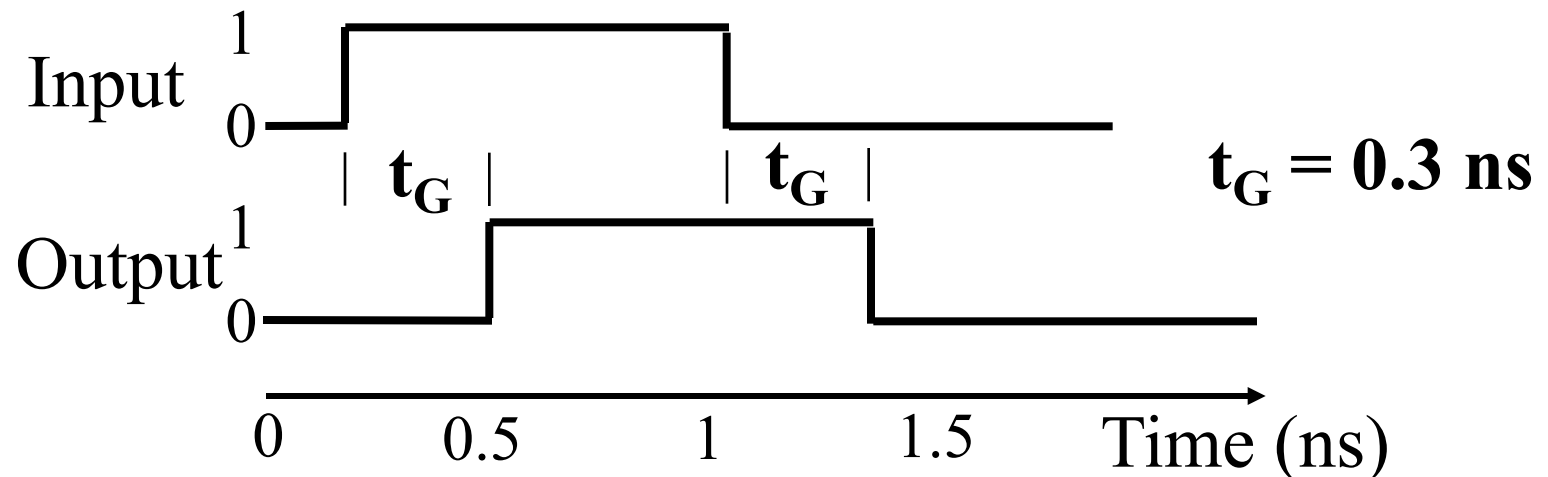
# Gate Delay

- In actual physical gates, if one or more input changes causes the output to change, the output change does not occur instantaneously.
- The delay between an input change(s) and the resulting output change is the *gate delay* denoted by  $t_G$ :



# Logic Diagrams and Expressions


**Truth Table**

<b>X Y Z</b>	<b><math>F = X + \bar{Y} \times Z</math></b>
0 0 0	0
0 0 1	1
0 1 0	0
0 1 1	0
1 0 0	1
1 0 1	1
1 1 0	1
1 1 1	1

**Equation**

$$F = X + \bar{Y} Z$$

**Logic Diagram**

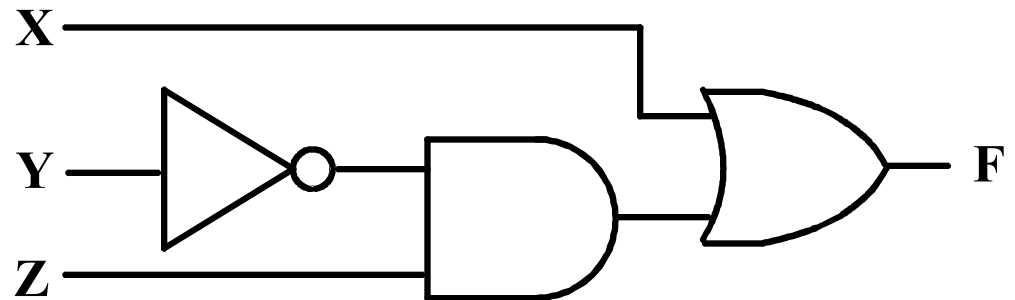

- Boolean equations, truth tables and logic diagrams describe the same function!
- Truth tables are unique; expressions and logic diagrams are not. This gives flexibility in implementing functions.

# Boolean Algebra

---

- An algebraic structure defined on a set of at least two elements,  $B$ , together with three binary operators (denoted  $+$ ,  $\cdot$  and  $\overline{\phantom{x}}$ ) that satisfies the following basic identities:

1.  $X + 0 = X$

2.  $X \cdot 1 = X$

3.  $X + 1 = 1$

4.  $X \cdot 0 = 0$

5.  $X + X = X$

6.  $X \cdot X = X$

7.  $X + \overline{X} = 1$

8.  $X \cdot \overline{X} = 0$

9.  $\overline{\overline{X}} = X$

---

10.  $X + Y = Y + X$

11.  $XY = YX$

Commutative

12.  $(X + Y) + Z = X + (Y + Z)$

13.  $(XY)Z = X(YZ)$

Associative

14.  $X(Y + Z) = XY + XZ$

15.  $X + YZ = (X + Y)(X + Z)$

Distributive

16.  $\overline{X + Y} = \overline{X} \cdot \overline{Y}$

17.  $\overline{X \cdot Y} = \overline{X} + \overline{Y}$

DeMorgan's

---



# Boolean Operator Precedence

---

- **The order of evaluation in a Boolean expression is:**
  1. Parentheses
  2. NOT
  3. AND
  4. OR
- **Consequence: Parentheses appear around OR expressions**
- **Example:  $F = A(B + C)(C + \overline{D})$**

# Some Properties of Identities & the Algebra

---

- If the meaning is unambiguous, we leave out the symbol “.”
- The identities above are organized into pairs. These pairs have names as follows:

1-4 Existence of 0 and 1

5-6 Idempotence

7-8 Existence of complement

9 Involution

10-11 Commutative Laws

12-13 Associative Laws

14-15 Distributive Laws

16-17 DeMorgan's Laws

- The dual of an algebraic expression is obtained by interchanging  $+$  and  $\cdot$  and interchanging 0's and 1's.
- The identities appear in dual pairs. When there is only one identity on a line the identity is self-dual, i. e., the dual expression = the original expression.

# Some Properties of Identities & the Algebra (Continued)

---

- Unless it happens to be self-dual, the dual of an expression does not equal the expression itself.
- Example:  $F = (A + \bar{C}) \cdot B + 0$   
 $\text{dual } F = (A \cdot \bar{C} + B) \cdot 1 = A \cdot \bar{C} + B$
- Example:  $G = X \cdot Y + \overline{(W + Z)}$   
 $\text{dual } G =$
- Example:  $H = A \cdot B + A \cdot C + B \cdot C$   
 $\text{dual } H =$
- Are any of these functions self-dual?

# Example 1: Boolean Algebraic Proof

---

- $A + A \cdot B = A$  (Absorption Theorem)

Proof Steps	Justification (identity or theorem)
-------------	-------------------------------------

$A + A \cdot B$	
-----------------	--

$= A \cdot 1 + A \cdot B$	$X = X \cdot 1$
---------------------------	-----------------

$= A \cdot (1 + B)$	$X \cdot Y + X \cdot Z = X \cdot (Y + Z)$ (Distributive Law)
---------------------	--

$= A \cdot 1$	$1 + X = 1$
---------------	-------------

$= A$	$X \cdot 1 = X$
-------	-----------------

- Our primary reason for doing proofs is to learn:
  - Careful and efficient use of the identities and theorems of Boolean algebra, and
  - How to choose the appropriate identity or theorem to apply to make forward progress, irrespective of the application.

## Example 2: Boolean Algebraic Proofs

---

- $AB + \bar{A}C + BC = AB + \bar{A}C$  (Consensus Theorem)

Proof Steps	Justification (identity or theorem)
-------------	-------------------------------------

$AB + \bar{A}C + BC$	
----------------------	--

$= AB + \bar{A}C + 1 \cdot BC$	?
--------------------------------	---

$= AB + \bar{A}C + (A + \bar{A}) \cdot BC$	?
--	---

$=$	
-----	--

# Example 3: Boolean Algebraic Proofs

---

- $(\overline{X + Y})Z + X\overline{Y} = \overline{Y}(X + Z)$

Proof Steps	Justification (identity or theorem)
-------------	-------------------------------------

$(\overline{X + Y})Z + X\overline{Y}$	
---------------------------------------	--

=	
---	--

# Useful Theorems

---

- $x \cdot y + \bar{x} \cdot y = y$      $(x + y)(\bar{x} + y) = y$     **Minimization**
- $x + x \cdot y = x$      $x \cdot (x + y) = x$     **Absorption**
- $x + \bar{x} \cdot y = x + y$      $x \cdot (\bar{x} + y) = x \cdot y$     **Simplification**
- $x \cdot y + \bar{x} \cdot z + y \cdot z = x \cdot y + \bar{x} \cdot z$     **Consensus**  
 $(x + y) \cdot (\bar{x} + z) \cdot (y + z) = (x + y) \cdot (\bar{x} + z)$
- $\overline{x + y} = \bar{x} \cdot \bar{y}$      $\overline{x \cdot y} = \bar{x} + \bar{y}$     **DeMorgan's Laws**

# Proof of Simplification

---

$$x \cdot y + \bar{x} \cdot y = y \quad (x + y)(\bar{x} + y) = y$$



# Boolean Function Evaluation

---

$$F1 = xy\bar{z}$$

$$F2 = x + \bar{y}z$$

$$F3 = \bar{x}\bar{y}\bar{z} + \bar{x}yz + x\bar{y}$$

$$F4 = x\bar{y} + \bar{x}z$$

x	y	z	F1	F2	F3	F4
0	0	0	0	0		
0	0	1	0	1		
0	1	0	0	0		
0	1	1	0	0		
1	0	0	0	1		
1	0	1	0	1		
1	1	0	1	1		
1	1	1	0	1		

# Expression Simplification

---

- An application of Boolean algebra
- Simplify to contain the smallest number of literals (complemented and uncomplemented variables):

$$\begin{aligned} & \mathbf{A B + \bar{A} C D + \bar{A} B D + \bar{A} C \bar{D} + A B C D} \\ &= \mathbf{A B + A B C D + \bar{A} C D + \bar{A} C \bar{D} + \bar{A} B D} \\ &= \mathbf{A B + A B (C D) + \bar{A} C (D + \bar{D}) + \bar{A} B D} \\ &= \mathbf{A B + \bar{A} C + \bar{A} B D = B(A + \bar{A} D) + \bar{A} C} \\ &= \mathbf{B (A + D) + \bar{A} C \quad 5 \text{ literals}} \end{aligned}$$

## Example: Simplify Expression

$$L = AB + \overline{A}\overline{C} + \overline{B}C + \overline{C}B + \overline{B}D + \overline{D}B + ADE(F + G) \text{ ———}$$

$$L = \overline{\overline{A}\overline{B}\overline{C}} + \overline{B}C + \overline{C}B + \overline{B}D + \overline{D}B + ADE(F + G) \quad \text{DeMorgan Laws}$$

$$= A + \overline{B}C + \overline{C}B + \overline{B}D + \overline{D}B + ADE(F + G) \quad A + \overline{A}B = A + B$$

$$= A + \overline{B}C + \overline{C}B + \overline{B}D + \overline{D}B \quad A + AB = A$$

$$= A + \overline{B}C(D + \overline{D}) + \overline{C}B + \overline{B}D + \overline{D}B(C + \overline{C}) \quad A + \overline{A} = 1$$

$$= A + \overline{B}CD + \overline{B}C\overline{D} + \overline{B}C + \overline{B}D + \overline{D}BC + \overline{D}B\overline{C} \quad \text{Distributive Laws}$$

$$= A + \overline{B}C\overline{D} + \overline{B}C + \overline{B}D + \overline{D}BC \quad A + AB = A$$

$$= A + \overline{C}\overline{D}(\overline{B} + B) + \overline{B}C + \overline{B}D$$

$$= A + \overline{C}\overline{D} + \overline{B}C + \overline{B}D \quad A + \overline{A} = 1$$

# Complementing Functions

---

- **Use DeMorgan's Theorem to complement a function:**
  1. Interchange AND and OR operators
  2. Complement each constant value and literal
- **Example: Complement  $F = \bar{x}y\bar{z} + x\bar{y}\bar{z}$**   
$$\bar{F} = (x + \bar{y} + z)(\bar{x} + y + z)$$
- **Example: Complement  $G = (\bar{a} + bc)\bar{d} + e$**   
$$\bar{G} =$$

# Overview – Canonical Forms

---

- **What are Canonical Forms?**
- **Minterms and Maxterms**
- **Index Representation of Minterms and Maxterms**
- **Sum-of-Minterm (SOM) Representations**
- **Product-of-Maxterm (POM) Representations**
- **Representation of Complements of Functions**
- **Conversions between Representations**

# Canonical Forms

---

- It is useful to specify Boolean functions in a form that:
  - Allows comparison for equality.
  - Has a correspondence to the truth tables
- Canonical Forms in common usage:
  - Sum of Minterms (SOM)
  - Product of Maxterms (POM)

# Minterms

---

- Minterms are AND terms with every variable present in either true or complemented form.
- Given that each binary variable may appear normal (e.g.,  $x$ ) or complemented (e.g.,  $\overline{x}$ ), there are  $2^n$  minterms for  $n$  variables.
- Example: Two variables ( $X$  and  $Y$ ) produce  $2 \times 2 = 4$  combinations:
  - $XY$  (both normal)
  - $X\overline{Y}$  ( $X$  normal,  $Y$  complemented)
  - $\overline{X}Y$  ( $X$  complemented,  $Y$  normal)
  - $\overline{X}\overline{Y}$  (both complemented)
- Thus there are four minterms of two variables.

# Maxterms

---

- Maxterms are OR terms with every variable in true or complemented form.
- Given that each binary variable may appear normal (e.g.,  $x$ ) or complemented (e.g.,  $\bar{x}$ ), there are  $2^n$  maxterms for  $n$  variables.
- Example: Two variables ( $X$  and  $Y$ ) produce  $2 \times 2 = 4$  combinations:

$X + Y$  (both normal)

$X + \bar{Y}$  ( $x$  normal,  $y$  complemented)

$\bar{X} + Y$  ( $x$  complemented,  $y$  normal)

$\bar{X} + \bar{Y}$  (both complemented)



# Maxterms and Minterms

---

- **Examples: Two variable minterms and maxterms.**

Index	Minterm	Maxterm
0	$\bar{x} \bar{y}$	$x + y$
1	$\bar{x} y$	$x + \bar{y}$
2	$x \bar{y}$	$\bar{x} + y$
3	$x y$	$\bar{x} + \bar{y}$

- **The index above is important for describing which variables in the terms are true and which are complemented.**

# Standard Order

- Minterms and maxterms are designated with a subscript
- The subscript is a number, corresponding to a binary pattern
- The bits in the pattern represent the complemented or normal state of each variable listed in a standard order.
- All variables will be present in a minterm or maxterm and will be listed in the same order (usually alphabetically)
- Example: For variables a, b, c:
  - Maxterms:  $(a + b + \bar{c})$ ,  $(a + b + c)$
  - Terms:  $(b + a + c)$ ,  $a \bar{c} b$ , and  $(c + b + a)$  are NOT in standard order.
  - Minterms:  $a \bar{b} c$ ,  $a b c$ ,  $\bar{a} \bar{b} c$
  - Terms:  $(a + c)$ ,  $\bar{b} c$ , and  $(\bar{a} + b)$  do not contain all variables

# Purpose of the Index

---

- The index for the minterm or maxterm, expressed as a binary number, is used to determine whether the variable is shown in the true form or complemented form.
- For Minterms:
  - “1” means the variable is “Not Complemented” and
  - “0” means the variable is “Complemented”.
- For Maxterms:
  - “0” means the variable is “Not Complemented” and
  - “1” means the variable is “Complemented”.

# Index Example in Three Variables

---

- **Example: (for three variables)**
- **Assume the variables are called X, Y, and Z.**
- **The standard order is X, then Y, then Z.**
- **The Index 0 (base 10) = 000 (base 2) for three variables). All three variables are complemented for minterm 0 (  $\bar{X}, \bar{Y}, \bar{Z}$ ) and no variables are complemented for Maxterm 0 (X,Y,Z).**
  - **Minterm 0, called  $m_0$  is  $\bar{X}\bar{Y}\bar{Z}$  .**
  - **Maxterm 0, called  $M_0$  is  $(X + Y + Z)$ .**
  - **Minterm 6 ?**
  - **Maxterm 6 ?**

# Index Examples – Four Variables

---

Index	Binary	Minterm	Maxterm
i	Pattern	$m_i$	$M_i$
0	0000	$\bar{a}\bar{b}\bar{c}\bar{d}$	$a + b + c + d$
1	0001	$\bar{a}\bar{b}\bar{c}d$	?
3	0011	?	$a + b + \bar{c} + \bar{d}$
5	0101	$\bar{a}b\bar{c}d$	$a + \bar{b} + c + \bar{d}$
7	0111	?	$a + \bar{b} + \bar{c} + \bar{d}$
10	1010	$a\bar{b}c\bar{d}$	$\bar{a} + b + \bar{c} + d$
13	1101	$ab\bar{c}d$	?
15	1111	$abcd$	$\bar{a} + \bar{b} + \bar{c} + \bar{d}$

# Minterm and Maxterm Relationship

---

- Review: DeMorgan's Theorem

$$\overline{x \cdot y} = \bar{x} + \bar{y} \text{ and } \overline{x + y} = \bar{x} \cdot \bar{y}$$

- Two-variable example:

$$M_2 = \bar{x} + y \text{ and } m_2 = x \cdot \bar{y}$$

Thus  $M_2$  is the complement of  $m_2$  and vice-versa.

- Since DeMorgan's Theorem holds for  $n$  variables, the above holds for terms of  $n$  variables
- giving:

$$M_i = \overline{m_i} \text{ and } m_i = \overline{M_i}$$

Thus  $M_i$  is the complement of  $m_i$ .

# Function Tables for Both

---

- **Minterms of 2 variables**

x y	$m_0$	$m_1$	$m_2$	$m_3$
0 0	1	0	0	0
0 1	0	1	0	0
1 0	0	0	1	0
1 1	0	0	0	1

## Maxterms of 2 variables

x y	$M_0$	$M_1$	$M_2$	$M_3$
0 0	0	1	1	1
0 1	1	0	1	1
1 0	1	1	0	1
1 1	1	1	1	0

- Each column in the maxterm function table is the complement of the column in the minterm function table since  $M_i$  is the complement of  $m_i$ .

# Observations

---

- In the function tables:
  - Each minterm has one and only one 1 present in the  $2^n$  terms (a minimum of 1s). All other entries are 0.
  - Each maxterm has one and only one 0 present in the  $2^n$  terms. All other entries are 1 (a maximum of 1s).
- We can implement any function by "ORing" the minterms corresponding to "1" entries in the function table. These are called the minterms of the function.
- We can implement any function by "ANDing" the maxterms corresponding to "0" entries in the function table. These are called the maxterms of the function.
- This gives us two canonical forms:
  - Sum of Minterms (SOM)
  - Product of Maxterms (POM)for stating any Boolean function.



# Minterm Function Example

- **Example: Find  $F_1 = m_1 + m_4 + m_7$**
- **$F_1 = \bar{x} \bar{y} z + x \bar{y} \bar{z} + x y z$**

x y z	index	$m_1 + m_4 + m_7 = F_1$					
0 0 0	0	0	+	0	+	0	= 0
0 0 1	1	1	+	0	+	0	= 1
0 1 0	2	0	+	0	+	0	= 0
0 1 1	3	0	+	0	+	0	= 0
1 0 0	4	0	+	1	+	0	= 1
1 0 1	5	0	+	0	+	0	= 0
1 1 0	6	0	+	0	+	0	= 0
1 1 1	7	0	+	0	+	1	= 1

# Minterm Function Example

---

- $F(A, B, C, D, E) = m_2 + m_9 + m_{17} + m_{23}$
- $F(A, B, C, D, E) =$

# Maxterm Function Example

- Example: Implement F1 in maxterms:

$$F_1 = M_0 \cdot M_2 \cdot M_3 \cdot M_5 \cdot M_6$$

$$F_1 = (x + y + z) \cdot (x + \bar{y} + z) \cdot (x + \bar{y} + \bar{z}) \cdot (\bar{x} + y + \bar{z}) \cdot (\bar{x} + \bar{y} + z)$$

x y z	i	$M_0 \cdot M_2 \cdot M_3 \cdot M_5 \cdot M_6 = F_1$
0 0 0	0	$0 \cdot 1 \cdot 1 \cdot 1 \cdot 1 = 0$
0 0 1	1	$1 \cdot 1 \cdot 1 \cdot 1 \cdot 1 = 1$
0 1 0	2	$1 \cdot 0 \cdot 1 \cdot 1 \cdot 1 = 0$
0 1 1	3	$1 \cdot 1 \cdot 0 \cdot 1 \cdot 1 = 0$
1 0 0	4	$1 \cdot 1 \cdot 1 \cdot 1 \cdot 1 = 1$
1 0 1	5	$1 \cdot 1 \cdot 1 \cdot 0 \cdot 1 = 0$
1 1 0	6	$1 \cdot 1 \cdot 1 \cdot 1 \cdot 0 = 0$
1 1 1	7	$1 \cdot 1 \cdot 1 \cdot 1 \cdot 1 = 1$

# Maxterm Function Example

---

- $F(A, B, C, D) = M_3 \cdot M_8 \cdot M_{11} \cdot M_{14}$
- $F(A, B, C, D) =$

# Canonical Sum of Minterms

---

- **Any Boolean function can be expressed as a Sum of Minterms.**
  - For the function table, the minterms used are the terms corresponding to the 1's
  - For expressions, expand all terms first to explicitly list all minterms. Do this by “ANDing” any term missing a variable  $v$  with a term  $(v + \bar{v})$ .
- **Example: Implement  $f = x + \bar{x} \bar{y}$  as a sum of minterms.**

First expand terms:  $f = x(y + \bar{y}) + \bar{x} \bar{y}$

Then distribute terms:  $f = xy + x\bar{y} + \bar{x} \bar{y}$

Express as sum of minterms:  $f = m_3 + m_2 + m_0$

# Another SOM Example

---

- **Example:  $F = A + \bar{B} C$**
- **There are three variables, A, B, and C which we take to be the standard order.**
- **Expanding the terms with missing variables:**
- **Collect terms (removing all but one of duplicate terms):**
- **Express as SOM:**

# Shorthand SOM Form

---

- From the previous example, we started with:

$$F = A + \bar{B} C$$

- We ended up with:

$$F = m_1 + m_4 + m_5 + m_6 + m_7$$

- This can be denoted in the formal shorthand:

$$F(A, B, C) = \Sigma_m(1, 4, 5, 6, 7)$$

- Note that we explicitly show the standard variables in order and drop the “m” designators.

# Canonical Product of Maxterms

- Any Boolean Function can be expressed as a Product of Maxterms (POM).
  - For the function table, the maxterms used are the terms corresponding to the 0's.
  - For an expression, expand all terms first to explicitly list all maxterms. Do this by first applying the second distributive law, “ORing” terms missing variable  $v$  with a term equal to  $v \cdot \bar{v}$  and then applying the distributive law again.

- Example: Convert to product of maxterms:

$$f(x, y, z) = x + \bar{x} \bar{y}$$

Apply the distributive law:

$$x + \bar{x} \bar{y} = (x + \bar{x})(x + \bar{y}) = 1 \cdot (x + \bar{y}) = x + \bar{y}$$

Add missing variable  $z$ :

$$x + \bar{y} + z \cdot \bar{z} = (x + \bar{y} + z)(x + \bar{y} + \bar{z})$$

Express as POM:  $f = M_2 \cdot M_3$



# Another POM Example

---

- Convert to Product of Maxterms:

$$f(A, B, C) = A \bar{C} + BC + \bar{A} \bar{B}$$

- Use  $x + yz = (x+y) \cdot (x+z)$  with  $x = (A \bar{C} + BC)$ ,  $y = \bar{A}$ , and  $z = \bar{B}$  to get:

$$f = (A \bar{C} + BC + \bar{A})(A \bar{C} + BC + \bar{B})$$

- Then use  $x + \bar{x}y = x + y$  to get:

$$f = (\bar{C} + BC + \bar{A})(A \bar{C} + C + \bar{B})$$

and a second time to get:

$$f = (\bar{C} + B + \bar{A})(A + C + \bar{B})$$

- Rearrange to standard order,

$$f = (\bar{A} + B + \bar{C})(A + \bar{B} + C) \text{ to give } f = M_5 \cdot M_2$$

# Function Complements

---

- The complement of a function expressed as a sum of minterms is constructed by selecting the minterms missing in the sum-of-minterms canonical forms.
- Alternatively, the complement of a function expressed by a Sum of Minterms form is simply the Product of Maxterms with the same indices.
- Example: Given  $F(x, y, z) = \Sigma_m(1, 3, 5, 7)$   
 $\bar{F}(x, y, z) = \Sigma_m(0, 2, 4, 6)$   
 $\bar{F}(x, y, z) = \Pi_M(1, 3, 5, 7)$

# Conversion Between Forms

---

- To convert between sum-of-minterms and product-of-maxterms form (or vice-versa) we follow these steps:
  - Find the function complement by swapping terms in the list with terms not in the list.
  - Change from products to sums, or vice versa.
- Example: Given  $F$  as before:  $F(x, y, z) = \Sigma_m(1, 3, 5, 7)$
- Form the Complement:  $\bar{F}(x, y, z) = \Sigma_m(0, 2, 4, 6)$
- Then use the other form with the same indices – this forms the complement again, giving the other form of the original function:  $F(x, y, z) = \Pi_M(0, 2, 4, 6)$

# Standard Forms

---

- Standard Sum-of-Products (SOP) form:  
equations are written as an OR of AND terms
- Standard Product-of-Sums (POS) form:  
equations are written as an AND of OR terms
- Examples:
  - SOP:  $A B C + \bar{A} \bar{B} C + B$
  - POS:  $(A + B) \cdot (A + \bar{B} + \bar{C}) \cdot C$
- These “mixed” forms are neither SOP nor POS
  - $(A B + C) (A + C)$
  - $A B \bar{C} + A C (A + B)$

# Standard Sum-of-Products (SOP)

---

- A sum of minterms form for  $n$  variables can be written down directly from a truth table.
  - Implementation of this form is a two-level network of gates such that:
  - The first level consists of  $n$ -input AND gates, and
  - The second level is a single OR gate (with fewer than  $2^n$  inputs).
- This form often can be simplified so that the corresponding circuit is simpler.

# Standard Sum-of-Products (SOP)

---

- A Simplification Example:

- $F(A, B, C) = \Sigma m(1, 4, 5, 6, 7)$

- Writing the minterm expression:

$$F = \overline{A} \overline{B} C + A \overline{B} \overline{C} + A \overline{B} C + A B \overline{C} + A B C$$



- Simplifying:

$$F =$$

- Simplified F contains 3 literals compared to 15 in minterm F
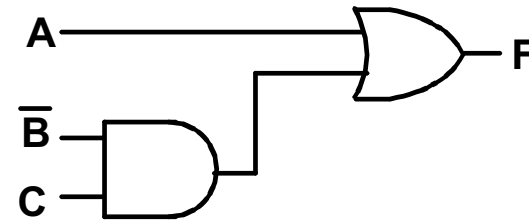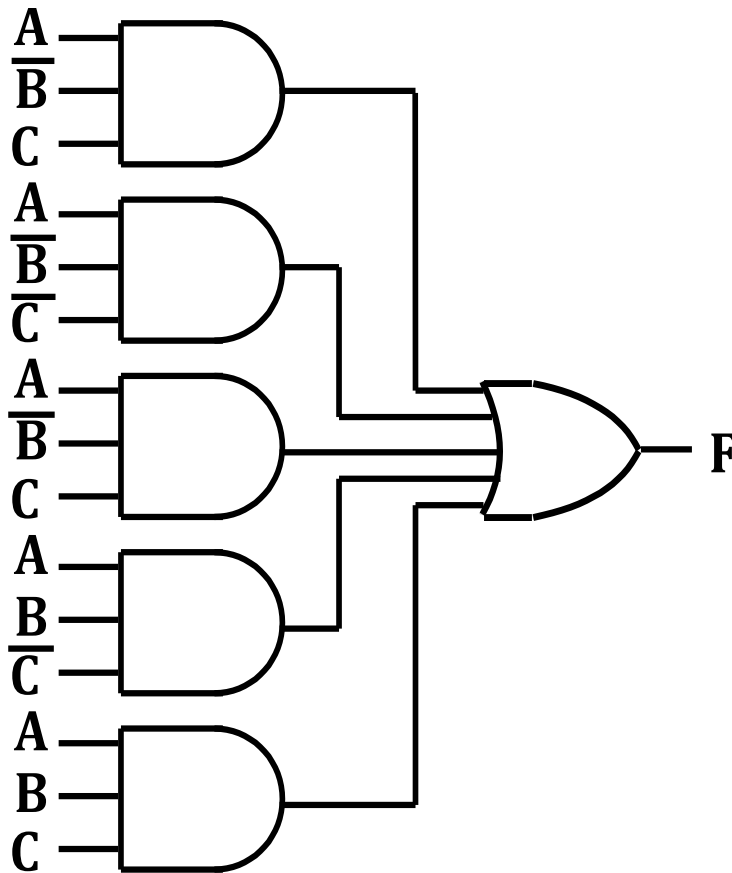
# AND/OR Two-level Implementation of SOP Expression

- The two implementations for  $F$  are shown below – it is quite apparent which is simpler!



# SOP and POS Observations

---

- **The previous examples show that:**
  - **Canonical Forms (Sum-of-minterms, Product-of-Maxterms), or other standard forms (SOP, POS) differ in complexity**
  - **Boolean algebra can be used to manipulate equations into simpler forms.**
  - **Simpler equations lead to simpler two-level implementations**
- **Questions:**
  - **How can we attain a “simplest” expression?**
  - **Is there only one minimum cost circuit?**
  - **The next part will deal with these issues.**



# Assignment

---

**2-1a; 2-2a, c; 2-3a, c; 2-6b, d; 2-10a, c; 2-11a, c, d; 2-12b**