

浙江大学

本科实验报告

课程名称:	计算机组成
姓 名:	姜雨童
学 院:	计算机科学与技术学院
专 业:	计算机科学与技术
邮 箱:	3220103450@zju.edu.cn
QQ 号:	1369218489
电 话:	19550103468
指导教师:	马德
报告日期:	2024 年 6 月 5 日

浙江大学实验报告

课程名称： 计算机组成 实验类型： 综合

实验项目名称： Lab 5: 流水线 CPU

学生姓名： 姜雨童 学号： 33220103450 同组学生姓名： /

实验地点： 紫金港东四 509 室 实验日期： 2024 年 6 月 5 日

一、操作方法与实验步骤


Lab5-1:流水线处理器集成

实验目的：

- 1.理解流水线 CPU 的基本原理和组织结构
- 2.掌握五级流水线的工作过程和设计方法
- 3.理解流水线 CPU 停机的原理
- 4.设计流水线测试程序

设计过程：

根据流水线集成设计图完成 Pipeline_CPU.v 文件的编写

 

代码如下所示（部分接口为后续 debug 时加上的，实验中并不做要求）：

Pipeline_CPU.v

```
module Pipeline_CPU (  
    input rst,  
    input clk,  
    input [31:0] Data_in,  
    input [31:0] Inst_IF,  
    output [31:0] PC_out_IF,  
    output [31:0] PC_out_ID,
```

```
output [31:0] PC_out_EX,
output [31:0] Inst_ID,
output [31:0] Addr_out,
output [31:0] Data_out,
output [31:0] Data_out_WB,
output MemRW_Mem,
output MemRW_EX,

output [31:0] zero,
output [31:0] ra,
output [31:0] sp,
output [31:0] gp,
output [31:0] tp,
output [31:0] t0,
output [31:0] t1,
output [31:0] t2,
output [31:0] s0,
output [31:0] s1,
output [31:0] a0,
output [31:0] a1,
output [31:0] a2,
output [31:0] a3,
output [31:0] a4,
output [31:0] a5,
output [31:0] a6,
output [31:0] a7,
output [31:0] s2,
output [31:0] s3,
output [31:0] s4,
output [31:0] s5,
output [31:0] s6,
output [31:0] s7,
output [31:0] s8,
output [31:0] s9,
output [31:0] s10,
output [31:0] s11,
output [31:0] t3,
output [31:0] t4,
output [31:0] t5,
output [31:0] t6,
output [31:0] Rs1_out_IDEX,
output [31:0] Rs2_out_IDEX,
output [31:0] Imm_out_IDEX
);
```

```

wire [31:0] PC_out_EXMem;
wire PCSrc;
wire RegWrite_out_MemWB;
wire [4:0] Rd_addr_out_MemWB;
wire [31:0] Rd_addr_out_ID;
wire [31:0] Rs1_out_ID;
wire [31:0] Rs2_out_ID;
wire [31:0] Imm_out_ID;
wire ALUSrc_B_ID;
wire [2:0] ALU_control_ID;
wire Branch_ID;
wire BranchN_ID;
wire MemRW_ID;
wire Jump_ID;
wire [1:0] MemtoReg_ID;
wire RegWrite_out_ID;
wire [31:0] PC_out_IDEX;
wire [4:0] Rd_addr_out_IDEX;
wire ALUSrc_B_out_IDEX;
wire [2:0] ALU_control_out_IDEX;
wire Branch_out_IDEX;
wire BranchN_out_IDEX;
wire Jump_out_IDEX;
wire [1:0] MemtoReg_out_IDEX;
wire RegWrite_out_IDEX;
wire [31:0] PC4_out_EX;
wire zero_out_EX;
wire [31:0] ALU_out_EX;
wire [31:0] Rs2_out_EX;
wire [31:0] PC4_out_EXMem;
wire [4:0] Rd_addr_out_EXMem;
wire zero_out_EXMem;
wire Branch_out_EXMem;
wire BranchN_out_EXMem;
wire Jump_out_EXMem;
wire [1:0] MemtoReg_out_EXMem;
wire RegWrite_out_EXMem;
wire [31:0] PC4_out_MemWB;
wire [31:0] ALU_out_MemWB;
wire [31:0] DMem_data_out_MemWB;
wire [1:0] MemtoReg_out_MemWB;

Pipeline_IF IF(
.clk_IF(clk),.rst_IF(rst),.en_IF(1'b1),

```

```

.PC_in_IF(PC_out_EXMem),.PCSrc(PCSrc),
.PC_out_IF(PC_out_IF)
);

IF_reg_ID IF_reg_ID(
.clk_IFID(clk),.rst_IFID(rst),.en_IFID(1'b1),
.PC_in_IFID(PC_out_IF),.inst_in_IFID(Inst_IF),
.PC_out_IFID(PC_out_ID),.inst_out_IFID(Inst_ID)
);

Pipeline_ID ID(
.clk_ID(clk),.rst_ID(rst),
.RegWrite_in_ID(RegWrite_out_MemWB),
.Rd_addr_ID(Rd_addr_out_MemWB),.Wt_data_ID(Data_out_WB),
.Inst_in_ID(Inst_ID),
.Rd_addr_out_ID(Rd_addr_out_ID),
.Rs1_out_ID(Rs1_out_ID),.Rs2_out_ID(Rs2_out_ID),
.Imm_out_ID(Imm_out_ID),
.ALUSrc_B_ID(ALUSrc_B_ID),.ALU_control_ID(ALU_control_ID),
.Branch_ID(Branch_ID),.BranchN_ID(BranchN_ID),
.MemRW_ID(MemRW_ID),.Jump_ID(Jump_ID),
.MemtoReg_ID(MemtoReg_ID),.RegWrite_out_ID(RegWrite_out_ID),
.zero(zero),
.ra(ra),
.sp(sp),
.gp(gp),
.tp(tp),
.t0(t0),
.t1(t1),
.t2(t2),
.s0(s0),
.s1(s1),
.a0(a0),
.a1(a1),
.a2(a2),
.a3(a3),
.a4(a4),
.a5(a5),
.a6(a6),
.a7(a7),
.s2(s2),
.s3(s3),
.s4(s4),
.s5(s5),

```

```

.s6(s6),
.s7(s7),
.s8(s8),
.s9(s9),
.s10(s10),
.s11(s11),
.t3(t3),
.t4(t4),
.t5(t5),
.t6(t6)
);

```

```

ID_reg_Ex ID_reg_Ex(
.clk_IDEX(clk),.rst_IDEX(rst),.en_IDEX(1'b1),
.PC_in_IDEX(PC_out_ID),
.Rd_addr_IDEX(Rd_addr_out_ID[4:0]),
.Rs1_in_IDEX(Rs1_out_ID),.Rs2_in_IDEX(Rs2_out_ID),
.Imm_in_IDEX(Imm_out_ID),
.ALUSrc_B_in_IDEX(ALUSrc_B_ID),.ALU_control_in_IDEX(ALU_control_ID),
.Branch_in_IDEX(Branch_ID),.BranchN_in_IDEX(BranchN_ID),
.MemRW_in_IDEX(MemRW_ID),.Jump_in_IDEX(Jump_ID),
.MemtoReg_in_IDEX(MemtoReg_ID),.RegWrite_in_IDEX(RegWrite_out_ID),
.PC_out_IDEX(PC_out_IDEX),
.Rd_addr_out_IDEX(Rd_addr_out_IDEX),
.Rs1_out_IDEX(Rs1_out_IDEX),.Rs2_out_IDEX(Rs2_out_IDEX),
.Imm_out_IDEX(Imm_out_IDEX),
.ALUSrc_B_out_IDEX(ALUSrc_B_out_IDEX),.ALU_control_out_IDEX(ALU_control_out_IDEX),
.Branch_out_IDEX(Branch_out_IDEX),.BranchN_out_IDEX(BranchN_out_IDEX),
.MemRW_out_IDEX(MemRW_EX),
.Jump_out_IDEX(Jump_out_IDEX),
.MemtoReg_out_IDEX(MemtoReg_out_IDEX),
.RegWrite_out_IDEX(RegWrite_out_IDEX)
);

```

```

Pipeline_Ex Ex(
.PC_in_EX(PC_out_IDEX),
.Rs1_in_EX(Rs1_out_IDEX),.Rs2_in_EX(Rs2_out_IDEX),
.Imm_in_EX(Imm_out_IDEX),
.ALUSrc_B_in_EX(ALUSrc_B_out_IDEX),
.ALU_control_in_EX(ALU_control_out_IDEX),
.PC_out_EX(PC_out_EX),
.PC4_out_EX(PC4_out_EX),
.zero_out_EX(zero_out_EX),
.ALU_out_EX(ALU_out_EX),

```

```
.Rs2_out_EX(Rs2_out_EX)
);
```

```
Ex_reg_Mem Ex_reg_Mem(
.clk_EXMem(clk),.rst_EXMem(rst),.en_EXMem(1'b1),
.PC_in_EXMem(PC_out_EX),.PC4_in_EXMem(PC4_out_EX),
.Rd_addr_EXMem(Rd_addr_out_IDEX),
.zero_in_EXMem(zero_out_EX),
.ALU_in_EXMem(ALU_out_EX),
.Rs2_in_EXMem(Rs2_out_EX),
.Branch_in_EXMem(Branch_out_IDEX),
.BranchN_in_EXMem(BranchN_out_IDEX),
.MemRW_in_EXMem(MemRW_EX),
.Jump_in_EXMem(Jump_out_IDEX),
.MemtoReg_in_EXMem(MemtoReg_out_IDEX),
.RegWrite_in_EXMem(RegWrite_out_IDEX),
.PC_out_EXMem(PC_out_EXMem),
.PC4_out_EXMem(PC4_out_EXMem),
.Rd_addr_out_EXMem(Rd_addr_out_EXMem),
.zero_out_EXMem(zero_out_EXMem),
.ALU_out_EXMem(Addr_out),
.Rs2_out_EXMem(Data_out),
.Branch_out_EXMem(Branch_out_EXMem),
.BranchN_out_EXMem(BranchN_out_EXMem),
.MemRW_out_EXMem(MemRW_Mem),
.Jump_out_EXMem(Jump_out_EXMem),
.MemtoReg_out_EXMem(MemtoReg_out_EXMem),
.RegWrite_out_EXMem(RegWrite_out_EXMem)
);
```

```
Pipeline_Mem Mem(
.zero_in_Mem(zero_out_EXMem),
.Branch_in_Mem(Branch_out_EXMem),
.BranchN_in_Mem(BranchN_out_EXMem),
.Jump_in_Mem(Jump_out_EXMem),
.PC Src(PCSrc)
);
```

```
Mem_reg_WB Mem_reg_WB(
.clk_MemWB(clk),.rst_MemWB(rst),.en_MemWB(1'b1),
.PC4_in_MemWB(PC4_out_EXMem),
.Rd_addr_MemWB(Rd_addr_out_EXMem),
.ALU_in_MemWB(Addr_out),
.DMem_data_MemWB(Data_in),
```

```

        .MemtoReg_in_MemWB(MemtoReg_out_EXMem),
        .RegWrite_in_MemWB(RegWrite_out_EXMem),
        .PC4_out_MemWB(PC4_out_MemWB),
        .Rd_addr_out_MemWB(Rd_addr_out_MemWB),
        .ALU_out_MemWB(ALU_out_MemWB),
        .DMem_data_out_MemWB(DMem_data_out_MemWB),
        .MemtoReg_out_MemWB(MemtoReg_out_MemWB),
        .RegWrite_out_MemWB(RegWrite_out_MemWB)
    );

    Pipeline_WB WB(
        .PC4_in_WB(PC4_out_MemWB),
        .ALU_in_WB(ALU_out_MemWB),
        .DMem_data_WB(DMem_data_out_MemWB),
        .MemtoReg_in_WB(MemtoReg_out_MemWB),
        .Data_out_WB(Data_out_WB)
    );
endmodule

```

后续将提供的模块（如 Pipeline_IF）导入（需要导入.v 和.edf 文件以实现模块功能），形成流水线集成 CPU 核，替换至 Lab2 所建立的 SOC 工程中并修改顶层文件中部分接口。修改后的顶层文件代码如下：

CSSTE.v

```

module CSSTE(
    input clk_100mhz,
    input RSTN,
    input [3:0] BTN_y,
    input [15:0] SW,
    output [3:0] Blue,
    output [3:0] Green,
    output [3:0] Red,
    output HSYNC,
    output VSYNC,
    output [15:0] LED_out,
    output [7:0] AN,
    output [7:0] segment
);
    wire [31:0] clkdiv;
    wire [31:0] PC_out;
    wire [15:0] SW_OK;
    wire [31:0] Addr_out;
    wire [31:0] Data_in;
    wire [31:0] Data_out;
    wire Clk_CPU;

```



```
wire [31:0] Inst_in;
wire rst;
wire [9:0] ram_addr;
wire [31:0] ram_data_in;
wire [31:0] RAM_B_0_douta;
wire U4_data_ram_we;
wire [3:0] BTN_OK;
wire [31:0] counter_out;
wire counter0_out;
wire counter1_out;
wire counter2_out;
wire U7_EN;
wire U5_EN;
wire counter_we;
wire [31:0] Peripheral_in;
wire [7:0] point;
wire [7:0] les;
wire [31:0] disp_num;
wire [1:0] counter_set;
wire [31:0] PC_out_ID;
wire [31:0] inst_ID;
wire [31:0] PC_out_EX;
wire MemRW_EX;
wire MemRW_Mem;
wire [31:0] Data_out_WB;

wire [31:0] zero;
wire [31:0] ra;
wire [31:0] sp;
wire [31:0] gp;
wire [31:0] tp;
wire [31:0] t0;
wire [31:0] t1;
wire [31:0] t2;
wire [31:0] s0;
wire [31:0] s1;
wire [31:0] a0;
wire [31:0] a1;
wire [31:0] a2;
wire [31:0] a3;
wire [31:0] a4;
wire [31:0] a5;
wire [31:0] a6;
wire [31:0] a7;
```

```

wire [31:0] s2;
wire [31:0] s3;
wire [31:0] s4;
wire [31:0] s5;
wire [31:0] s6;
wire [31:0] s7;
wire [31:0] s8;
wire [31:0] s9;
wire [31:0] s10;
wire [31:0] s11;
wire [31:0] t3;
wire [31:0] t4;
wire [31:0] t5;
wire [31:0] t6;
wire [31:0] Rs1_out_IDEX;
wire [31:0] Rs2_out_IDEX;
wire [31:0] Imm_out_IDEX;

```

Pipeline_CPU U1

```

(.clk(Clk_CPU),.rst(rst),
 .Inst_IF(Inst_in),
 .Data_in(Data_in),
 .PC_out_IF(PC_out),
 .PC_out_ID(PC_out_ID),
 .Inst_ID(inst_ID),
 .PC_out_EX(PC_out_EX),
 .MemRW_EX(MemRW_EX),
 .MemRW_Mem(MemRW_Mem),
 .Data_out(Data_out),
 .Addr_out(Addr_out),
 .Data_out_WB(Data_out_WB),
 .zero(zero),
 .ra(ra),
 .sp(sp),
 .gp(gp),
 .tp(tp),
 .t0(t0),
 .t1(t1),
 .t2(t2),
 .s0(s0),
 .s1(s1),
 .a0(a0),
 .a1(a1),
 .a2(a2),

```

```

.a3(a3),
.a4(a4),
.a5(a5),
.a6(a6),
.a7(a7),
.s2(s2),
.s3(s3),
.s4(s4),
.s5(s5),
.s6(s6),
.s7(s7),
.s8(s8),
.s9(s9),
.s10(s10),
.s11(s11),
.t3(t3),
.t4(t4),
.t5(t5),
.t6(t6),
.Rs1_out_IDEX(Rs1_out_IDEX),
.Rs2_out_IDEX(Rs2_out_IDEX),
.Imm_out_IDEX(Imm_out_IDEX)
);

```

ROM U2

```

(.a(PC_out[11:2]),.spo(Inst_in));

```

RAM U3

```

(.addra(ram_addr),.clka(~clk_100mhz),.dina(ram_data_in),
.douta(RAM_B_0_douta),.wea(U4_data_ram_we));

```

MIO_BUS U4

```

(.clk(clk_100mhz),.rst(rst),.BTN(BTN_OK),.SW(SW_OK),
.mem_w(MemRW_Mem),.Cpu_data2bus(Data_out),.addr_bus(Addr_out),
.ram_data_out(RAM_B_0_douta),.led_out(LED_out),.counter_out(counter_out),
.counter0_out(counter0_out),.counter1_out(counter1_out),.counter2_out(counter2_o
ut),
.Cpu_data4bus(Data_in),.ram_data_in(ram_data_in),.ram_addr(ram_addr),
.data_ram_we(U4_data_ram_we),.GPIOf0000000_we(U7_EN),.GPIOe0000000_we(U5_EN),
.counter_we(counter_we),.Peripheral_in(Peripheral_in));

```

Multi_8CH32 U5

```

(.clk(~Clk_CPU),.rst(rst),.EN(U5_EN),.Test(SW_OK[7:5]),

```

```

        .point_in({clkdiv,clkdiv}),.LES(64'b0),.Data0(Peripheral_in),.data1({2'b0,PC_out
[31:2]}),
        .data2(Inst_in),.data3(counter_out),.data4(Addr_out),.data5(Data_out),
        .data6(Data_in),.data7(PC_out),
        .point_out(point),.LE_out(les),.Disp_num(dis_num));

Seg7_Dev_0 U6
    (.disp_num(disp_num),.point(point),.les(les),.scan(clkdiv[18:16]),
    .AN(AN),.segment(segment));

SPI0 U7
    (.clk(~Clk_CPU),.rst(rst),.Start(clkdiv[20]),.EN(U7_EN),.P_Data(Peripheral_in),
    .counter_set(counter_set),.LED_out(LED_out));

clk_div U8
    (.clk(clk_100mhz),.rst(rst),.SW2(SW_OK[2]),.SW8(SW_OK[8]),.STEP(SW_OK[10]),
    .clkdiv(clkdiv),.Clk_CPU(Clk_CPU));

SAnti_jitter U9
    (.clk(clk_100mhz),.RSTN(RSTN),.readn(1'b0),.Key_y(BTN_y),.SW(SW),
    .rst(rst),.BTN_OK(BTN_OK),.SW_OK(SW_OK));

Counter_x U10
    (.clk(~Clk_CPU),.rst(rst),.clk0(clkdiv[6]),.clk1(clkdiv[9]),.clk2(clkdiv[11]),
    .counter_we(counter_we),.counter_val(Peripheral_in),.counter_ch(counter_set),
    .counter0_OUT(counter0_out),.counter1_OUT(counter1_out),.counter2_OUT(counter2_o
ut),
    .counter_out(counter_out));

VGA U11
    (.clk_25m(clkdiv[1]),.clk_100m(clk_100mhz),.rst(rst),
    .PC_IF(PC_out),.inst_IF(Inst_in),
    .PC_ID(PC_out_ID),.inst_ID(inst_ID),
    .PC_Ex(PC_out_EX),
    .MemRW_Ex(MemRW_EX),
    .MemRW_Mem(MemRW_Mem),
    .Data_out(Data_out),
    .Addr_out(Addr_out),
    .Data_out_WB(Data_out_WB),
    .hs(HSYNC),.vs(VSYNC),.vga_r(Red),.vga_g(Green),.vga_b(Blue),
    .zero(zero),
    .ra(ra),
    .sp(sp),
    .gp(gp),


```

```

        .tp(tp),
        .t0(t0),
        .t1(t1),
        .t2(t2),
        .s0(s0),
        .s1(s1),
        .a0(a0),
        .a1(a1),
        .a2(a2),
        .a3(a3),
        .a4(a4),
        .a5(a5),
        .a6(a6),
        .a7(a7),
        .s2(s2),
        .s3(s3),
        .s4(s4),
        .s5(s5),
        .s6(s6),
        .s7(s7),
        .s8(s8),
        .s9(s9),
        .s10(s10),
        .s11(s11),
        .t3(t3),
        .t4(t4),
        .t5(t5),
        .t6(t6),
        .Rs1_out_IDEX(Rs1_out_IDEX),
        .Rs2_out_IDEX(Rs2_out_IDEX),
        .Imm_out_IDEX(Imm_out_IDEX)
    );
endmodule

```

集成完成之后，工程层次如下图所示：

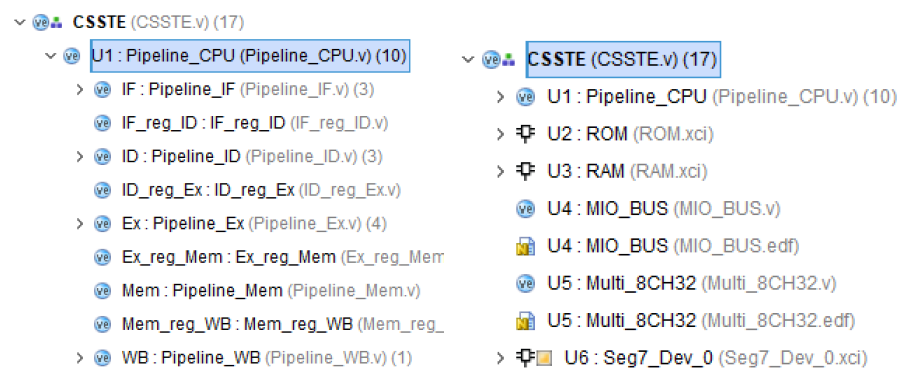

后续生成 bit 文件，上板验证集成环境是否建立成功。

Lab5-2:流水线 CPU 实现（不含 hazard）


实验目的：

- 1.理解流水线 CPU 的基本原理和组织结构
- 2.掌握五级流水线的工作过程和设计方法
- 3.理解流水线的设计原理
- 4.设计流水线测试程序

设计过程：

根据相应的接口和该模块的功能，编写 verilog 代码实现

Pipeline_IF.v:

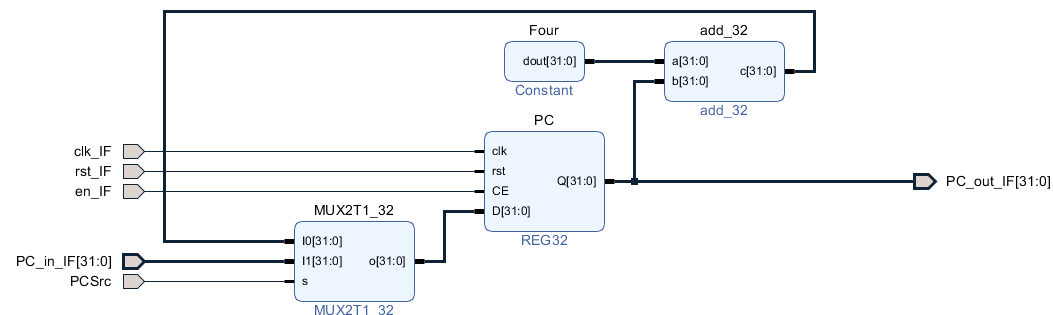

```
module Pipeline_IF(  
    input clk_IF,  
    input rst_IF,  
    input en_IF,  
    input [31:0] PC_in_IF,  
    input PCSrc,  
    output [31:0] PC_out_IF  
);  
    wire [31:0] mux_out;  
    wire [31:0] add_out;  
  
    MUX2T1_32 MUX(  
        .I0(add_out),  
        .I1(PC_in_IF),  
        .s(PCSrc),  
        .o(mux_out)  
    );  
  
    REG32 PC(  
        .clk(clk_IF),  
        .rst(rst_IF),  
        .CE(en_IF),  
        .D(mux_out),  
        .Q(PC_out_IF)  
    );  
    add_32 add_32(  
        .a(Four),  
        .b(PC_out_IF),  
        .c(add_out)  
    );  
endmodule
```

```


.D(mux_out),
.Q(PC_out_IF)
);

ADD32 ADD(
.a(32'h00000004),
.b(PC_out_IF),
.o(add_out)
);

```

Endmodule

Pipeline_ID.v:

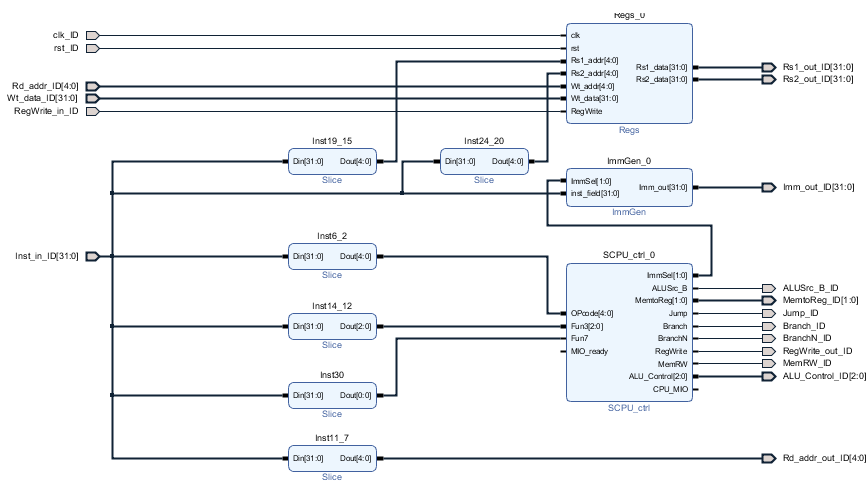

```

module Pipeline_ID(
    input clk_ID,
    input rst_ID,
    input RegWrite_in_ID,
    input [4:0] Rd_addr_ID,
    input [31:0] Wt_data_ID,
    input [31:0] Inst_in_ID,
    output [31:0] Rd_addr_out_ID,
    output [31:0] Rs1_out_ID,
    output [31:0] Rs2_out_ID,
    output [31:0] Imm_out_ID,
    output ALUSrc_B_ID,
    output [2:0] ALU_control_ID,
    output Branch_ID,
    output BranchN_ID,
    output MemRW_ID,
    output Jump_ID,
    output [1:0] MemtoReg_ID,
    output RegWrite_out_ID,

```

```

output [31:0] zero,
output [31:0] ra,
output [31:0] sp,
output [31:0] gp,
output [31:0] tp,
output [31:0] t0,
output [31:0] t1,
output [31:0] t2,
output [31:0] s0,
output [31:0] s1,
output [31:0] a0,
output [31:0] a1,
output [31:0] a2,
output [31:0] a3,
output [31:0] a4,
output [31:0] a5,
output [31:0] a6,
output [31:0] a7,
output [31:0] s2,
output [31:0] s3,
output [31:0] s4,
output [31:0] s5,
output [31:0] s6,
output [31:0] s7,
output [31:0] s8,
output [31:0] s9,
output [31:0] s10,
output [31:0] s11,
output [31:0] t3,
output [31:0] t4,
output [31:0] t5,
output [31:0] t6
);

wire [2:0] ImmSel; /**
assign Rd_addr_out_ID[4:0] = Inst_in_ID[11:7];

regs regs(
.clk(clk_ID),
.rst(rst_ID),
.Rs1_addr(Inst_in_ID[19:15]),
.Rs2_addr(Inst_in_ID[24:20]),
.Wt_addr(Rd_addr_ID),
.Wt_data(Wt_data_ID),

```



```

.RegWrite(RegWrite_in_ID),
.Rs1_data(Rs1_out_ID),
.Rs2_data(Rs2_out_ID),
.zero(zero),
.ra(ra),
.sp(sp),
.gp(gp),
.tp(tp),
.t0(t0),
.t1(t1),
.t2(t2),
.s0(s0),
.s1(s1),
.a0(a0),
.a1(a1),
.a2(a2),
.a3(a3),
.a4(a4),
.a5(a5),
.a6(a6),
.a7(a7),
.s2(s2),
.s3(s3),
.s4(s4),
.s5(s5),
.s6(s6),
.s7(s7),
.s8(s8),
.s9(s9),
.s10(s10),
.s11(s11),
.t3(t3),
.t4(t4),
.t5(t5),
.t6(t6)
);

```

```

ImmGen ImmGen(
.ImmSel(ImmSel),
.inst_field(Inst_in_ID),
.Imm_out(Imm_out_ID)
);

```

```

SCPU_ctr1 SCPU_ctr1(


```

```

.OpcodE(Inst_in_ID[6:2]),
.Fun3(Inst_in_ID[14:12]),
.Fun7(Inst_in_ID[30]),
.ImmSel(ImmSel),
.ALUSrc_B(ALUSrc_B_ID),
.MemtoReg(MemtoReg_ID),
.Jump(Jump_ID),
.Branch(Branch_ID),
.BranchN(BranchN_ID),
.RegWrite(RegWrite_out_ID),
.MemRW(MemRW_ID),
.ALU_Control(ALU_control_ID)
);
endmodule

```

Pipeline_Ex.v:

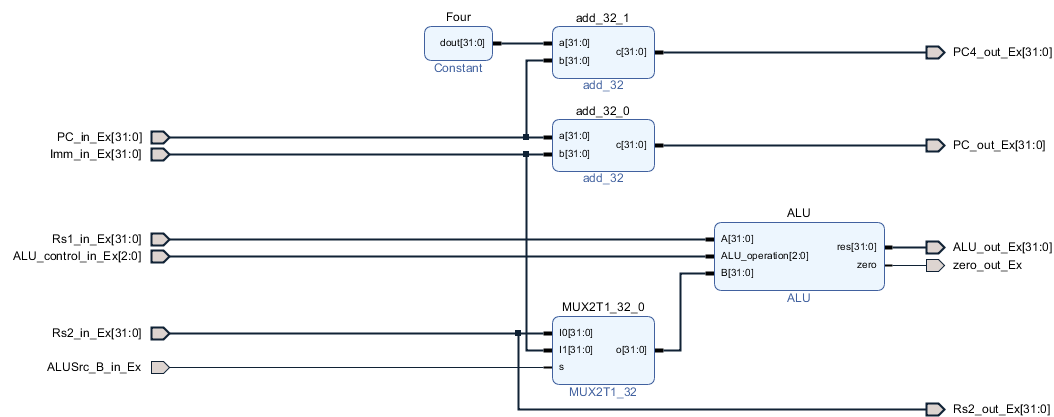

```

module Pipeline_Ex(
    input[31:0] PC_in_EX,
    input[31:0] Rs1_in_EX,
    input[31:0] Rs2_in_EX,
    input[31:0] Imm_in_EX,
    input ALUSrc_B_in_EX,
    input[2:0] ALU_control_in_EX,
    output wire [31:0] PC_out_EX,
    output wire [31:0] PC4_out_EX,
    output wire zero_out_EX,
    output wire [31:0] ALU_out_EX,
    output wire [31:0] Rs2_out_EX
);

    wire [31:0] mux_out;

    assign Rs2_out_EX = Rs2_in_EX;

```

```

ADD32 ADD1(
    .a(32'h00000004),
    .b(PC_in_EX),
    .o(PC4_out_EX)
);


ADD32 ADD2(
    .a(PC_in_EX),
    .b(Imm_in_EX),
    .o(PC_out_EX)
);

MUX2T1_32 MUX(
    .I0(Rs2_in_EX),
    .I1(Imm_in_EX),
    .s(ALUSrc_B_in_EX),
    .o(mux_out)
);

ALU ALU(
    .A(Rs1_in_EX),
    .B(mux_out),
    .ALU_operation(ALU_control_in_EX),
    .res(ALU_out_EX),
    .zero(zero_out_EX)
);
endmodule

```

Pipeline_Mem.v:

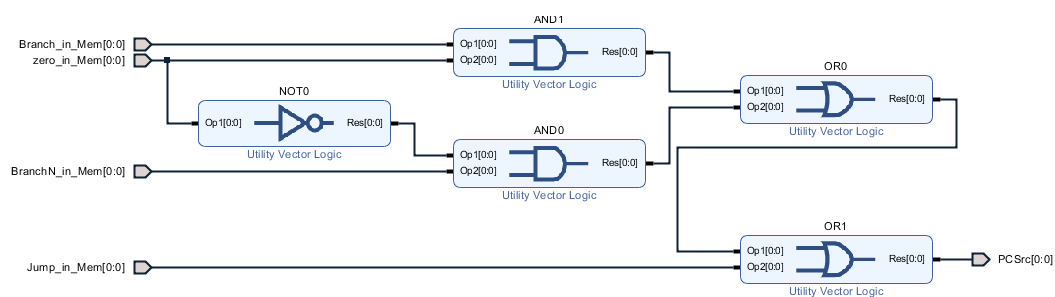

```

module Pipeline_Mem(
    input zero_in_Mem,
    input Branch_in_Mem,
    input BranchN_in_Mem,
    input Jump_in_Mem,
    output PCSrc
)

```

```


    );

    assign PCSrc = Jump_in_Mem | (Branch_in_Mem & zero_in_Mem) | ((~zero_in_Mem) &
BranchN_in_Mem);

endmodule

```

Pipeline_WB.v:

 

```

module Pipeline_WB(
    input [31:0] PC4_in_WB,
    input [31:0] ALU_in_WB,
    input [31:0] DMem_data_WB,
    input [1:0] MemtoReg_in_WB,
    output [31:0] Data_out_WB
);

    MUX4T1_32 MUX(
        .s(MemtoReg_in_WB),
        .I0(ALU_in_WB),
        .I1(DMem_data_WB),
        .I2(PC4_in_WB),
        .I3(PC4_in_WB),
        .o(Data_out_WB)
    );

endmodule

```

IF_reg_ID.v:

```

module IF_reg_ID(
    input clk_IFID,
    input rst_IFID,
    input en_IFID,
    input [31:0] PC_in_IFID,
    input [31:0] inst_in_IFID,
    output reg [31:0] PC_out_IFID,
    output reg [31:0] inst_out_IFID
);

```

```

always @(posedge clk_IFID or posedge rst_IFID)
    if (rst_IFID == 1'b1) begin
        PC_out_IFID <= 32'h00000000;
        inst_out_IFID <= 32'h00000000;
    end
    else if(en_IFID == 1'b0) begin
        PC_out_IFID <= PC_out_IFID;
        inst_out_IFID <= inst_out_IFID;
    end
    else begin
        PC_out_IFID <= PC_in_IFID;
        inst_out_IFID <= inst_in_IFID;
    end
endmodule

```

ID_reg_Ex.v:

```

module ID_reg_Ex(
    input clk_IDEX,
    input rst_IDEX,
    input en_IDEX,
    input [31:0] PC_in_IDEX,
    input [4:0] Rd_addr_IDEX,
    input [31:0] Rs1_in_IDEX,
    input [31:0] Rs2_in_IDEX,
    input [31:0] Imm_in_IDEX ,
    input ALUSrc_B_in_IDEX ,
    input [2:0] ALU_control_in_IDEX,
    input Branch_in_IDEX,
    input BranchN_in_IDEX,
    input MemRW_in_IDEX,
    input Jump_in_IDEX, /*
    input [1:0] MemtoReg_in_IDEX,
    input RegWrite_in_IDEX,
    output reg [31:0] PC_out_IDEX,
    output reg [4:0] Rd_addr_out_IDEX,
    output reg [31:0] Rs1_out_IDEX,
    output reg [31:0] Rs2_out_IDEX,
    output reg [31:0] Imm_out_IDEX ,
    output reg ALUSrc_B_out_IDEX ,
    output reg [2:0] ALU_control_out_IDEX,
    output reg Branch_out_IDEX,
    output reg BranchN_out_IDEX,
    output reg MemRW_out_IDEX,
    output reg Jump_out_IDEX, /*

```

```

        output reg [1:0] MemtoReg_out_IDEX,
        output reg RegWrite_out_IDEX
    );

    always @(posedge clk_IDEX or posedge rst_IDEX) begin
        if (rst_IDEX == 1'b1) begin
            PC_out_IDEX <= 32'b0;
            Rs1_out_IDEX <= 32'b0;
            Rs2_out_IDEX <= 32'b0;
            Imm_out_IDEX <= 32'b0;
            Rd_addr_out_IDEX <= 5'b0;
            ALUSrc_B_out_IDEX <= 1'b0;
            ALU_control_out_IDEX <= 3'b0;
            Branch_out_IDEX <= 1'b0;
            BranchN_out_IDEX <= 1'b0;
            MemRW_out_IDEX <= 1'b0;
            Jump_out_IDEX <= 1'b0;
            MemtoReg_out_IDEX <= 2'b0;
            RegWrite_out_IDEX <= 1'b0;
        end
        else if (en_IDEX) begin
            PC_out_IDEX <= PC_in_IDEX;
            Rs1_out_IDEX <= Rs1_in_IDEX;
            Rs2_out_IDEX <= Rs2_in_IDEX;
            Imm_out_IDEX <= Imm_in_IDEX;
            Rd_addr_out_IDEX <= Rd_addr_IDEX;
            ALUSrc_B_out_IDEX <= ALUSrc_B_in_IDEX;
            ALU_control_out_IDEX <= ALU_control_in_IDEX;
            Branch_out_IDEX <= Branch_in_IDEX;
            BranchN_out_IDEX <= BranchN_in_IDEX;
            MemRW_out_IDEX <= MemRW_in_IDEX;
            Jump_out_IDEX <= Jump_in_IDEX;
            MemtoReg_out_IDEX <= MemtoReg_in_IDEX;
            RegWrite_out_IDEX <= RegWrite_in_IDEX;
        end
    end
endmodule

```

Ex_reg_Mem.v:

```

module Ex_reg_Mem(
    input clk_EXMem,
    input rst_EXMem,
    input en_EXMem,
    input [31:0] PC_in_EXMem,

```

```

    input [31:0] PC4_in_EXMem,
    input [4:0] Rd_addr_EXMem,
    input zero_in_EXMem,
    input [31:0] ALU_in_EXMem,
    input [31:0] Rs2_in_EXMem,
    input Branch_in_EXMem,
    input BranchN_in_EXMem,
    input MemRW_in_EXMem,
    input Jump_in_EXMem, /*
    input [1:0] MemtoReg_in_EXMem,
    input RegWrite_in_EXMem,
    output reg [31:0] PC_out_EXMem,
    output reg [31:0] PC4_out_EXMem,
    output reg [4:0] Rd_addr_out_EXMem,
    output reg zero_out_EXMem,
    output reg [31:0] ALU_out_EXMem,
    output reg [31:0] Rs2_out_EXMem,
    output reg Branch_out_EXMem,
    output reg BranchN_out_EXMem,
    output reg MemRW_out_EXMem,
    output reg Jump_out_EXMem, /*
    output reg [1:0] MemtoReg_out_EXMem,
    output reg RegWrite_out_EXMem
);

```

```

always @(posedge clk_EXMem or posedge rst_EXMem)

```

```

    if (rst_EXMem == 1'b1) begin
        PC_out_EXMem <= 32'b0;
        PC4_out_EXMem <= 32'b0;
        Rd_addr_out_EXMem <= 5'b0;
        zero_out_EXMem <= 1'b0;
        ALU_out_EXMem <= 32'b0;
        Rs2_out_EXMem <= 32'b0;
        Branch_out_EXMem <= 1'b0;
        BranchN_out_EXMem <= 1'b0;
        MemRW_out_EXMem <= 1'b0;
        Jump_out_EXMem <= 1'b0;
        MemtoReg_out_EXMem <= 2'b0;
        RegWrite_out_EXMem <= 1'b0;
    end
    else if (en_EXMem == 1'b1) begin
        PC_out_EXMem <= PC_in_EXMem;
        PC4_out_EXMem <= PC4_in_EXMem;
        Rd_addr_out_EXMem <= Rd_addr_EXMem;

```

```

    zero_out_EXMem <= zero_in_EXMem;
    ALU_out_EXMem <= ALU_in_EXMem;
    Rs2_out_EXMem <= Rs2_in_EXMem;
    Branch_out_EXMem <= Branch_in_EXMem;
    BranchN_out_EXMem <= BranchN_in_EXMem;
    MemRW_out_EXMem <= MemRW_in_EXMem;
    Jump_out_EXMem <= Jump_in_EXMem;
    MemtoReg_out_EXMem <= MemtoReg_in_EXMem;
    RegWrite_out_EXMem <= RegWrite_in_EXMem;
    end
endmodule

```

Mem_reg_WB.v:

```

module Mem_reg_WB(
    input clk_MemWB,
    input rst_MemWB,
    input en_MemWB,
    input [31:0] PC4_in_MemWB,
    input [4:0] Rd_addr_MemWB,
    input [31:0] ALU_in_MemWB,
    input [31:0] DMem_data_MemWB,
    input [1:0] MemtoReg_in_MemWB,
    input RegWrite_in_MemWB,
    output reg [31:0] PC4_out_MemWB,
    output reg [4:0] Rd_addr_out_MemWB,
    output reg [31:0] ALU_out_MemWB,
    output reg [31:0] DMem_data_out_MemWB,
    output reg [1:0] MemtoReg_out_MemWB,
    output reg RegWrite_out_MemWB
);

always @(posedge clk_MemWB or posedge rst_MemWB)
    if (rst_MemWB == 1'b1) begin
        PC4_out_MemWB <= 32'b0;
        Rd_addr_out_MemWB <= 5'b0;
        ALU_out_MemWB <= 32'b0;
        DMem_data_out_MemWB <= 32'b0;
        MemtoReg_out_MemWB <= 2'b0;
        RegWrite_out_MemWB <= 1'b0;
    end
    else if (en_MemWB == 1'b1) begin
        PC4_out_MemWB <= PC4_in_MemWB;
        Rd_addr_out_MemWB <= Rd_addr_MemWB;
        ALU_out_MemWB <= ALU_in_MemWB;
    end
end

```



```

        DMem_data_out_MemWB <= DMem_data_MemWB;
        MemtoReg_out_MemWB <= MemtoReg_in_MemWB;
        RegWrite_out_MemWB <= RegWrite_in_MemWB;

    end

endmodule

```

全部模块编写完成后, 替换 lab5-1 中提供的各模块 ip 核, 集成流水线 CPU。(此处为了 debug, 额外添加了寄存器等接口, 因此代码行数较多。) 生成 bit 文件后, 上板验证,

Lab5-3:流水线 CPU 实现 (含 hazard)

截至本报告提交时, 我还没有写出能跑通 hazard 的流水线 CPU, 因此把现有的含有 bug 的源代码放在报告末尾处。(当前版本的代码, 跑含 hazard 的指令 h.coe 时行为表现与不含冒险的代码基本一致, 因此不在实验结果分析模块另外说明上板结果。)


二、实验结果与分析

不含 hazard 版本 (p.coe):


经过逐步比对, 该流水线 CPU 的行为完全符合预期。

本报告内为了便于说明, 只截取程序结束时的两个连续时钟周期, 通过比对 ID 阶段各寄存器的值和期望值来说明流水线符合预期。(因为提供的观察接口并没有全部接入, 因此图中有部分数据是观察不到并且默认为零的。这里将几个接入的数据标出, 便于观察。)

PC = 0x8c:

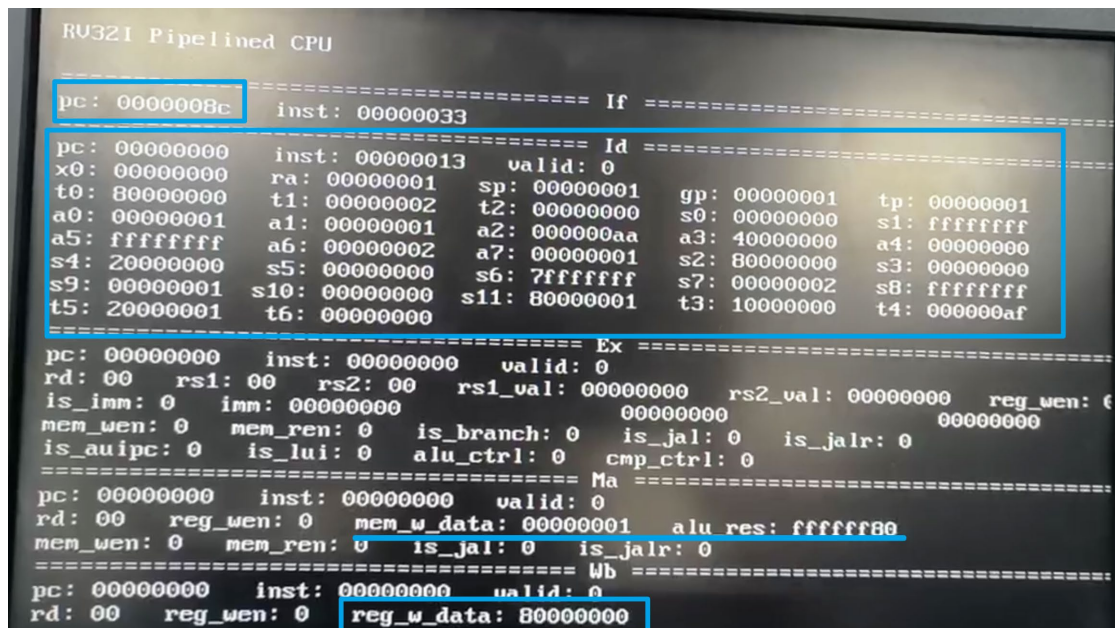

PC = 0x00:

 

可以看到,图一中ID阶段显示寄存器t6的值还未写入,为零;而WB阶段返回数据reg_w_data为0x80000000,恰好为下一指令执行时被写回t6的数据。

更多的验证结果可以比对ID阶段各寄存器的值和下方的指令(0x68处andi指令的结果在图上标错了,现用粉色字迹更正,)

PC	Machine Code	Basic Code	Original Code	Result
0x0	0x00100093	addi x1 x0 1	main: addi x1,x0,0x1	#x1 = 0x1
0x4	0x00100113	addi x2 x0 1	addi x2,x0,0x1	#x2 = 0x1
0x8	0x00100193	addi x3 x0 1	addi x3,x0,0x1	#x3 = 0x1
0xc	0x00100213	addi x4 x0 1	addi x4,x0,0x1	#x4 = 0x1
0x10	0x00802283	lw x5 8(x0)	lw x5,0x8(x0)	#x5 = 0x80000000
0x14	0x00108333	add x6 x1 x1	add x6,x1,x1	#x6 = 0x2
0x18	0x0020C3B3	xor x7 x1 x2	xor x7,x1,x2	#x7 = 0
0x1c	0x40110433	sub x8 x2 x1	sub x8,x2,x1	#x8 = 0
0x20	0x05C02483	lw x9 92(x0)	lw x9,0x5c(x0)	#x9 = 0xFFFFFFFF
0x24	0x00327533	and x10 x4 x3	and x10,x4,x3	#x10 = 0x1
0x28	0x00502223	sw x5 4(x0)	sw x5,0x4(x0)	#mem(1)= 0x80000000
0x2c	0x005325B3	slt x11 x6 x5	slt x11,x6,x5	#x11 = 0x1
0x30	0x0AA3C613	xori x12 x7 170	xori x12,x7,0xAA	#x12 = 0xAA
0x34	0x0012D6B3	srl x13 x5 x1	srl x13,x5,x1	#X13 = 0x40000000
0x38	0x00147713	andi x14 x8 1	andi x14,x8,0x1	#x14 = 0
0x3c	0x0034E7B3	or x15 x9 x3	or x15,x9,x3	#x15 = 0xFFFFFFFF
0x40	0x00A50833	add x16 x10 x10	add x16,x10,x10	#x16 = 0x2
0x44	0x0085C8B3	xor x17 x11 x8	xor x17,x11,x8	#x17 = 0x1
0x48	0x00402903	lw x18 4(x0)	lw x18,0x4(x0)	#x18 = 0x80000000
0x4c	0x004629B3	slt x19 x12 x4	slt x19,x12,x4	#x19 = 0
0x50	0x0016DA13	srli x20 x13 1	srli x20,x13,0x1	#x20 = 0x20000000
0x54	0x00677AB3	and x21 x14 x6	and x21,x14,x6	#x21 = 0
0x58	0x40128B33	sub x22 x5 x1	sub x22,x5,x1	#x22 = 0x7FFFFFFF
0x5c	0x00150B93	addi x23 x10 1	addi x23,x10,0x1	#x23 = 0x2
0x60	0x00986C33	or x24 x16 x9	or x24,x16,x9	#x24 = 0xFFFFFFFF
0x64	0x00B9CCB3	xor x25 x19 x11	xor x25,x19,x11	#x25 = 0x1
0x68	0x0FFA7D13	andi x26 x20 255	andi x26,x20,0xFF	#x26 = 0x200000FF
0x6c	0x00390DB3	add x27 x18 x3	add x27,x18,x3	#x27 = 0x80000001
0x70	0x002A5E33	srl x28 x20 x2	srl x28,x20,x2	#x28 = 0x10000000
0x74	0x0AF9EE93	ori x29 x19 175	ori x29,x19,0xAF	#x29 = 0xAF
0x78	0x001A0F33	add x30 x20 x1	add x30,x20,x1	#x30 = 0x20000001
0x7c	0x00802F83	lw x31 8(x0)	lw x31,0x8(x0)	#x31 = 0x80000000

含 hazard 版本 (h.coe):

(因为我并没有写出能跑通的 CPU, 这里仅给出不能跑通的结果并进行分析。)

下图是跑的指令, 其中橙色标记处是和我的流水线 CPU 表现结果相比有出入的地方:

1. 0x14 处指令是第一次出现冒险的位置, 由于上一条指令写回寄存器 x5, 本条指令使用寄存器 x5 内的值, 而实际上在 (未能实现 hazard 功能的) 流水线 CPU 内, 上一条指令还没经过 WB 阶段, 寄存器 x5 内的值还未更正, 因此值出现不同。
2. 而在跳转指令处 (如 0x34), 流水线还未跳转便获取了下一条指令, 导致中间个别本不该执行的指令也一并执行。
3. 几个有箭头的位置表明, 上一步寄存器没有存放正确的值导致这一步结果出错 (但是带入寄存器内实际值时, 这几条指令都是正常执行的。)
4. 寄存器 t6 内没有值是因为实际跑的指令没有 0x90 这一条。

PC	Machine Code	Basic Code	Original Code	Result
0x0	0x00100093	addi x1 x0 1	main: addi x1,x0,0x1	#x1 = 0x1
0x4	0x00100113	addi x2 x0 1	addi x2,x0,0x1	#x2 = 0x1
0x8	0x00100193	addi x3 x0 1	addi x3,x0,0x1	#x3 = 0x1
0xc	0x00100213	addi x4 x0 1	addi x4,x0,0x1	#x4 = 0x1
0x10	0x00802283	lw x5 8(x0)	lw x5,0x8(x0)	#x5 = 0x80000000
0x14	0x00128333	add x6 x5 x1	add x6,x5,x1	#x6 = 0x80000001
0x18	0x0020C3B3	xor x7 x1 x2	xor x7,x1,x2	#x7 = 0
0x1c	0x40708433	sub x8 x1 x7	sub x8,x1,x7	#x8 = 0x1
0x20	0x05C02483	lw x9 92(x0)	lw x9,0x5c(x0)	#x9 = 0xFFFFFFFF
0x24	0x00327533	and x10 x4 x3	and x10,x4,x3	#x10= 0x1
0x28	0x00502223	sw x5 4(x0)	sw x5,0x4(x0)	#mem(1)= 0x80000000
0x2c	0x005325B3	slt x11 x6 x5	slt x11,x6,x5	#x11= 0x0
0x30	0x0AA3C613	xori x12 x7 170	xori x12,x7,0xAA	#x12= 0xAA
0x34	0x00818663	beq x3 x8 12	beq x3,x8,loop1	
0x38	0x00000013	addi x0 x0 0	addi x0,x0,0x0	
0x3c	0x00000033	add x0 x0 x0	add x0,x0,x0	
0x40	0x0012D6B3	srl x13 x5 x1	loop1:srl x13,x5,x1	#x13= 0x40000000
0x44	0x00147713	andi x14 x8 1	andi x14,x8,0x1	#x14= 0x1
0x48	0x0034E7B3	or x15 x9 x3	or x15,x9,x3	#x15= 0xFFFFFFFF
0x4c	0x00A50833	add x16 x10 x10	add x16,x10,x10	#x16= 0x2
0x50	0x0085C8B3	xor x17 x11 x8	xor x17,x11,x8	#x17= 0x1
0x54	0x00402903	lw x18 4(x0)	lw x18,0x4(x0)	#x18= 0x80000000
0x58	0x004629B3	slt x19 x12 x4	slt x19,x12,x4	#x19= 0
0x5c	0x0016DA13	srl x20 x13 1	srl x20,x13,0x1	#x20= 0x20000000
0x60	0x00677AB3	and x21 x14 x6	and x21,x14,x10	#x21= 0x1
0x64	0x01071463	bne x14 x16 8	bne x14,x12,loop2	
0x68	0x00000013	addi x0 x0 0	addi x0,x0,0x0	
0x6c	0x40128B33	sub x22 x5 x1	loop2:sub x22,x5,x1	#x22= 0x7FFFFFFF
0x70	0x00150B93	addi x23 x10 1	addi x23,x10,0x1	#x23= 0x2
0x74	0x00986C33	or x24 x16 x9	or x24,x16,x9	#x24= 0xFFFFFFFF
0x78	0x00B9CCB3	xor x25 x19 x11	xor x25,x19,x11	#x25= 0x0
0x7c	0x0FFA7D13	andi x26 x20 255	andi x26,x20,0xFF	#x26= 0x200000FF
0x80	0x00390DB3	add x27 x18 x3	add x27,x18,x3	#x27= 0x80000001
0x84	0x002A5E33	srl x28 x20 x2	srl x28,x20,x2	#x28= 0x10000000
0x88	0x0AF9EE93	ori x29 x19 175	ori x29,x19,0xAF	#x29= 0xAF
0x8c	0x001A0F33	add x30 x20 x1	add x30,x20,x1	#x30= 0x20000001
0x90	0x00802F83	lw x31 8(x0)	lw x31,0x8(x0)	#x31= 0x80000000
0x94	0xF6DFF06F	jal x0 -148	jal x0,main	

下面是实际流水线 CPU 实际跑的结果:

图一处，0x38 指令本该被跳过。

图二 ID 阶段的寄存器可以用来比对上述结果。


```
RU32I Pipelined CPU
===== If =====
pc: 00000038 inst: 00000013
===== Id =====
pc: 00000034 inst: 00818663 valid: 0
x0: 00000000 ra: 00000001 sp: 00000001 gp: 00000001 tp: 00000001
t0: 80000000 t1: 00000001 t2: 00000000 s0: 00000001 s1: ffffffff
a0: 00000001 a1: 00000000 a2: 00000000 a3: 00000000 a4: 00000000
a5: 00000000 a6: 00000000 a7: 00000000 s2: 00000000 s3: 00000000
s4: 00000000 s5: 00000000 s6: 00000000 s7: 00000000 s8: 00000000
s9: 00000000 s10: 00000000 s11: 00000000 t3: 00000000 t4: 00000000
t5: 00000000 t6: 00000000
===== Ex =====
pc: 000000da inst: 00000000 valid: 0
rd: 00 rs1: 00 rs2: 00 rs1_val: 00000000 rs2_val: 00000000 reg_wen: 0
```

```
RU32I Pipelined CPU
===== If =====
pc: 000000a8 inst: 00000000
===== Id =====
pc: 000000a4 inst: 00000000 valid: 0
x0: 00000000 ra: 00000001 sp: 00000001 gp: 00000001 tp: 00000001
t0: 80000000 t1: 00000001 t2: 00000000 s0: 00000001 s1: ffffffff
a0: 00000001 a1: 00000001 a2: 000000aa a3: 40000000 a4: 00000001
a5: ffffffff a6: 00000002 a7: 00000000 s2: 80000000 s3: 00000000
s4: 20000000 s5: 00000001 s6: 7fffffff s7: 00000002 s8: ffffffff
s9: 00000001 s10: 00000000 s11: 80000001 t3: 10000000 t4: 000000af
t5: 20000001 t6: 00000000
===== Ex =====
pc: 000000a0 inst: 00000000 valid: 0
rd: 00 rs1: 00 rs2: 00 rs1_val: 00000000 rs2_val: 00000000 reg_wen: 0
is_imm: 0 imm: 00000000 00000000
mem_wen: 0 mem_ren: 0 is_branch: 0 is_jal: 0 is_jalr: 0
is_auiopc: 0 is_lui: 0 alu_ctrl: 0 cmp_ctrl: 0
===== Ma =====
pc: 00000000 inst: 00000000 valid: 0
rd: 00 reg_wen: 0 mem_w_data: 00000000 alu_res: 00000000
mem_wen: 0 mem_ren: 0 is_jal: 0 is_jalr: 0
===== Wb =====
pc: 00000000 inst: 00000000 valid: 0
rd: 00 reg_wen: 0 reg_w_data: f0000000
```


三、讨论、心得

本次实验非常非常的麻烦，也非常非常的困难！很遗憾截至上交报告时，还是没有写出正确的含冒险的流水线 CPU。过程中记录的一些报错和解决办法如下：

1. 执行的时候出现报错（如图）：

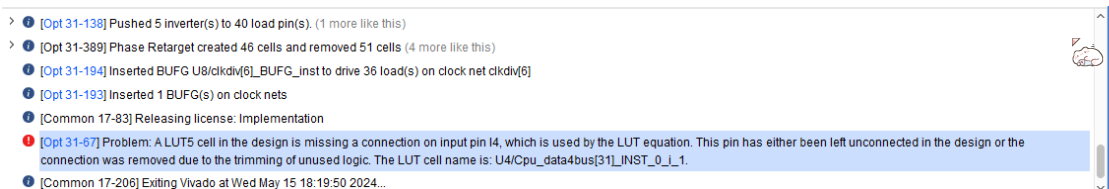

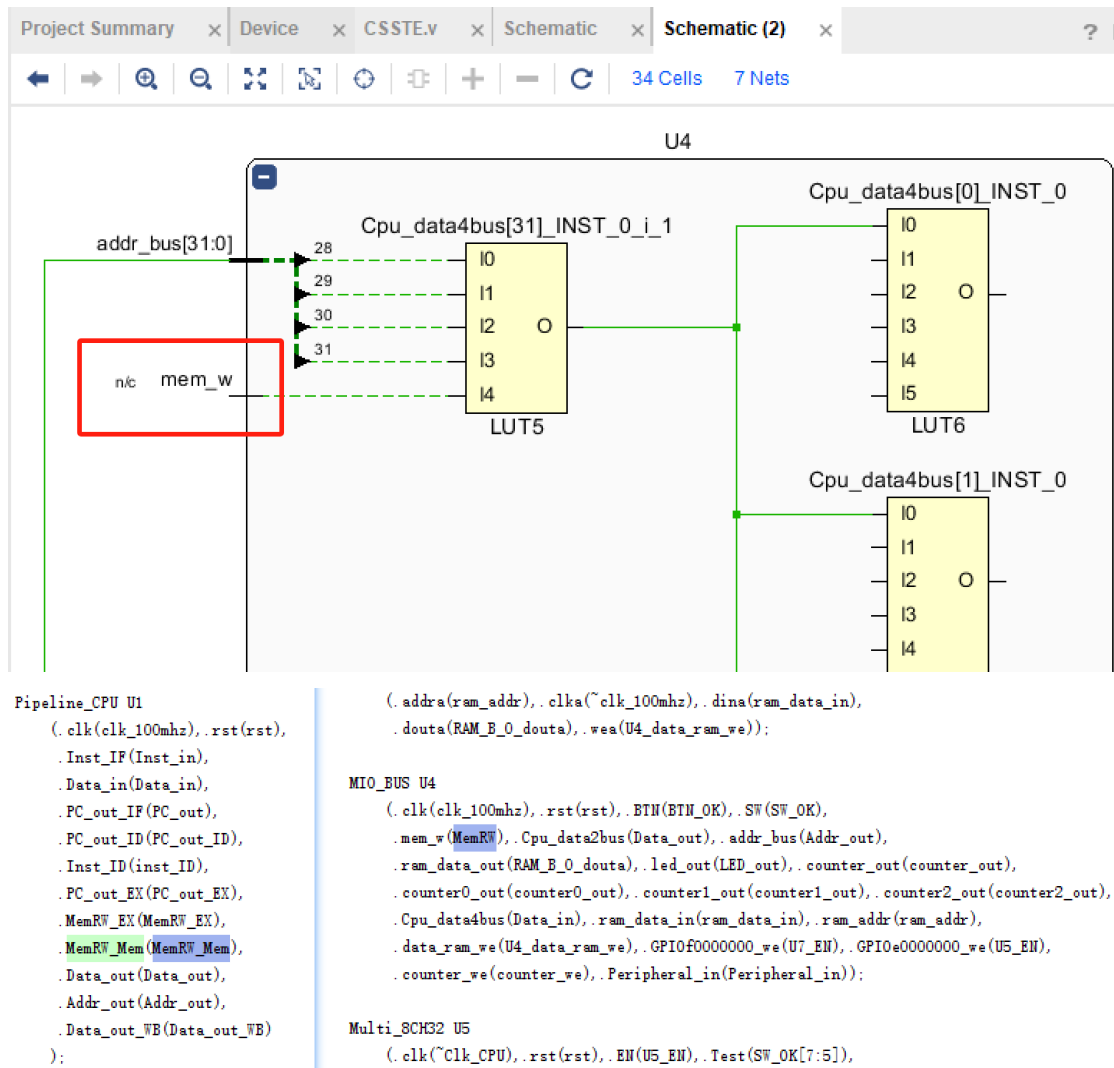先是根据网上的信息（https://support.xilinx.com/s/article/72980?language=en_US）进行排查，发现 U4 模块线没接好（如下图 1）。改正后仍有错误，最后发现是命名不一致导致的（如下图二）。



2. 下图所示报错:

Synthesis (5 critical warnings)

synth_1 (5 critical warnings)


[Synth 8-4442] BlackBox module \U1\ID has unconnected pin Rd_addr_ID[4] (4 more like this)

- [Synth 8-4442] BlackBox module \U1\ID has unconnected pin Rd_addr_ID[3]
- [Synth 8-4442] BlackBox module \U1\ID has unconnected pin Rd_addr_ID[2]
- [Synth 8-4442] BlackBox module \U1\ID has unconnected pin Rd_addr_ID[1]
- [Synth 8-4442] BlackBox module U9 has unconnected pin readn

Implementation (1 error)

检查后发现是信号的位宽有错（因此上图报错没有报 0 位）

 3. 在 lab5-1 阶段, 最初上板时显示非常奇怪 (vga 显示的数字疯狂闪动, 没有固定值; 板上则是不管怎么改变 SW 开关, 七段管显示的数据都没有任何变化):



检查后发现是 CPU 信号接错了（应该是 Clk_CPU，如图）

```

Pipeline_CPU U1
  (.clk(Clk_CPU), .rst(rst),
   .Inst_IF(Inst_in),
   .Data_in(Data_in),

```

- 此外还有一个常见错误就是信号的位数接错了。

四、个人生活照片



五、debug 版本 hazard 流水线

```

module stall(
  input rst_stall,
  input [4:0]Rs1_addr_ID,
  input [4:0]Rs2_addr_ID,
  input RegWrite_out_IDEX,
  input RegWrite_out_EXMem,

```

```

input [4:0]Rd_addr_out_IDEX,
input [4:0]Rd_addr_out_EXMem,
input Rs1_used,
input Rs2_used,
input Branch_ID,
input BranchN_ID,
input Jump_ID, /*
input Branch_out_IDEX,
input BranchN_out_IDEX,
input Jump_out_IDEX,
input Branch_out_EXMem,
input BranchN_out_EXMem,
input Jump_out_EXMem,
output reg en_IF,
output reg en_IFID,
output reg NOP_IFID,
output reg NOP_IDEX
);\

/* data hazard */
reg Data_stall;
always @(*) begin
    if(RegWrite_out_EXMem && Rs1_used && (Rs1_addr_ID != 5'b0) && (Rd_addr_out_EXMem
== Rs1_addr_ID))
        Data_stall = 1'b1;
    else if(RegWrite_out_EXMem && Rs2_used && (Rs2_addr_ID != 5'b0) &&
(Rd_addr_out_EXMem == Rs2_addr_ID))
        Data_stall = 1'b1;
    else if(RegWrite_out_IDEX && Rs1_used && (Rs1_addr_ID != 5'b0) &&
(Rd_addr_out_IDEX == Rs1_addr_ID))
        Data_stall = 1'b1;
    else if(RegWrite_out_IDEX && Rs2_used && (Rs2_addr_ID != 5'b0) &&
(Rd_addr_out_IDEX == Rs2_addr_ID))
        Data_stall = 1'b1;
    else
        Data_stall = 1'b0;
end

/* Control hazard */
reg Control_stall;
always @(*) begin
    if((Branch_ID || BranchN_ID || Jump_ID) || (Branch_out_IDEX || BranchN_out_IDEX
|| Jump_out_IDEX) || (Branch_out_EXMem || BranchN_out_EXMem || Jump_out_EXMem))
        Control_stall = 1'b1;

```

```

        else
            Control_stall = 1'b0;
        end

/* stall */
always @(*) begin
    if(rst_stall == 1'b1) begin
        en_IF = 1'b1;
        en_IFID = 1'b1;
        NOP_IDEX = 1'b0;
        NOP_IFID = 1'b0;
    end else begin
        if (Control_stall == 1'b1)
            NOP_IFID = 1'b1;    //Insert nop
        else
            NOP_IFID = 1'b0;
            if (Data_stall == 1'b1) begin
                en_IF = 1'b0;
                en_IFID = 1'b0;    //Hold pc and if/id reg
                NOP_IDEX = 1'b1;    //insert nop and disable REGWrite,MemRW
            end else begin
                en_IF = 1'b1;
                en_IFID = 1'b1;
                NOP_IDEX = 1'b0;
            end
        end
    end
end
endmodule

```