
Computer Logic Design Fundamentals

Chapter 5 – Digital Hardware Implementation

Part 2 – Programmable Implementation Technologies

Prof. Yueming Wang

ymingwang@zju.edu.cn

College of Computer Science and Technology,
Zhejiang University

Overview

- **Part 1 – The Design Space**
- **Part 2 - Programmable Implementation Technologies**
 - **Why Programmable Logic?**
 - **Programming Technologies**
 - **Read-Only Memories (ROMs)**
 - **Programmable Logic Arrays (PLAs)**
 - **Programmable Array Logic (PALs)**

Why Programmable Logic?

- **Facts:**

- It is most economical to produce an IC in large volumes
- Many designs required only small volumes of ICs

- **Need an IC that can be:**

- Produced in large volumes
- Handle many designs required in small volumes

- **A programmable logic part can be:**

- made in large volumes
- programmed to implement large numbers of different low-volume designs

Programmable Logic - More Advantages

- Many programmable logic devices are *field-programmable*, i. e., can be programmed outside of the manufacturing environment
- Most programmable logic devices are *erasable* and *reprogrammable*.
 - Allows “updating” a device or correction of errors
 - Allows reuse the device for a different design - the ultimate in re-usability!
 - Ideal for course laboratories
- Programmable logic devices can be used to prototype design that will be implemented for sale in regular ICs.
 - Complete Intel Pentium designs were actually prototyped with specialized systems based on large numbers of VLSI programmable devices!

Programming Technologies

- **Programming technologies are used to:**
 - **Control connections**
 - **Build lookup tables**
 - **Control transistor switching**
- **The technologies**
 - **Control connections**
 - **Mask programming**
 - **Fuse**
 - **Antifuse**
 - **Single-bit storage element**

Programming Technologies

- **The technologies (continued)**
 - **Build lookup tables**
 - **Storage elements (as in a memory)**
 - **Transistor Switching Control**
 - **Stored charge on a floating transistor gate**
 - Erasable
 - Electrically erasable
 - Flash (as in Flash Memory)
 - **Storage elements (as in a memory)**


Technology Characteristics

- **Permanent - Cannot be erased and reprogrammed**
 - Mask programming
 - Fuse
 - Antifuse
- **Reprogrammable**
 - **Volatile - Programming lost if chip power lost**
 - Single-bit storage element
 - **Non-Volatile**
 - Erasable
 - Electrically erasable
 - Flash (as in Flash Memory)


Programmable Configurations

- ***Read Only Memory (ROM)*** - a fixed array of AND gates and a programmable array of OR gates
- ***Programmable Array Logic (PAL)***[®] - a programmable array of AND gates feeding a fixed array of OR gates.
- ***Programmable Logic Array (PLA)*** - a programmable array of AND gates feeding a programmable array of OR gates.
- ***Complex Programmable Logic Device (CPLD) /Field- Programmable Gate Array (FPGA)*** - complex enough to be called “architectures” - See VLSI Programmable Logic Devices reading supplement


ROM, PAL and PLA Configurations

 

(a) Programmable read-only memory (PROM)

 

 (b) Programmable array logic (PAL) device



(c) Programmable logic array (PLA) device

Read Only Memory


- **Read Only Memories (ROM) or Programmable Read Only Memories (PROM) have:**
 - **N input lines,**
 - **M output lines, and**
 - **2^N decoded minterms.**
- **Fixed AND array with 2^N outputs implementing all N-literal minterms.**
- **Programmable OR Array with M outputs lines to form up to M sum of minterm expressions.**

Read Only Memory

- A program for a ROM or PROM is simply a multiple-output truth table
 - If a 1 entry, a connection is made to the corresponding minterm for the corresponding output
 - If a 0, no connection is made
- Can be viewed as a *memory* with the inputs as *addresses* of *data* (output values), hence ROM or PROM names!

Read Only Memory Example

 - Example: A 8 X 4 ROM (N = 3 input lines, M= 4 output lines)
- The fixed "AND" array is a “decoder” with 3 inputs and 8 outputs implementing minterms.
- The programmable “OR” array uses a single line to represent all inputs to an OR gate. An “X” in the array corresponds to attaching the minterm to the OR
- Read Example: For input $(A_2, A_1, A_0) = 001$, output is $(F_3, F_2, F_1, F_0) = 0011$.
- What are functions F_3, F_2, F_1 and F_0 in terms of (A_2, A_1, A_0) ?



Example: Square of 3-bit input number


Inputs			Outputs						
A_2	A_1	A_0	B_5	B_4	B_3	B_2	B_1	B_0	Decimal
0	0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	1	1
0	1	0	0	0	0	1	0	0	4
0	1	1	0	0	1	0	0	1	9
1	0	0	0	1	0	0	0	0	16
1	0	1	0	1	1	0	0	1	25
1	1	0	1	0	0	1	0	0	36
1	1	1	1	1	0	0	0	1	49

$$B_0 = A_0$$

$$B_1 = 0$$

 Example: Square of 3-bit input number

- **8 × 4 ROM are selected ROM Truth Table**



A ₂	A ₁	A ₀	B ₅	B ₄	B ₃	B ₂
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	1
0	1	1	0	0	1	0
1	0	0	0	1	0	0
1	0	1	0	1	1	0
1	1	0	1	0	0	1
1	1	1	1	1	0	0

Programmable Array Logic (PAL)

- **The PAL is the opposite of the ROM, having a programmable set of ANDs combined with fixed ORs.**
- **Disadvantage**
 - **ROM guaranteed to implement any M functions of N inputs. PAL may have too few inputs to the OR gates.**
- **Advantages**
 - **For given internal complexity, a PAL can have larger N and M**
 - **Some PALs have outputs that can be complemented, adding POS functions**
 - **No multilevel circuit implementations in ROM (without external connections from output to input). PAL has outputs from OR terms as internal inputs to all AND terms, making implementation of multi-level circuits easier.**

Programmable Array Logic Example


- 4-input, 4-output PAL with fixed, 3-input OR terms
- What are the equations for F1 through F4?

$$F1 = \overline{A}\overline{B} + \overline{C}$$

$$F2 = \overline{A}B\overline{C} + AC + A\overline{B}$$

$$F3 =$$

$$F4 =$$

 

Programmable Array Logic

- **Design requires fitting functions within the limited number of ANDs per OR gate**
- **Single function optimization is the first step to fitting**
- **Otherwise, if the number of terms in a function is greater than the number of ANDs per OR gate, then factoring is necessary**

Programmable Array Logic Example


- Equations: $F1 = A\bar{B}\bar{C} + \bar{A}B\bar{C} + \bar{A}\bar{B}C + ABC$
 $F2 = AB + BC + AC$

- F1 must be factored since four terms

- Factor out last two terms as W

Product term	AND Inputs					Outputs
	A	B	C	D	W	
1	0	0	1	—	—	$W = \bar{A}\bar{B}C + ABC$
2	1	1	1	—	—	
3	—	—	—	—	—	
4	1	0	0	—	—	$F1 = X = \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + W$
5	0	1	0	—	—	
6	—	—	—	—	1	
7	1	1	—	—	—	$F2 = Y = AB + BC + AC$
8	—	1	1	—	—	
9	1	—	1	—	—	
10	—	—	—	—	—	
11	—	—	—	—	—	
12	—	—	—	—	—	

Programmable Array Logic Example

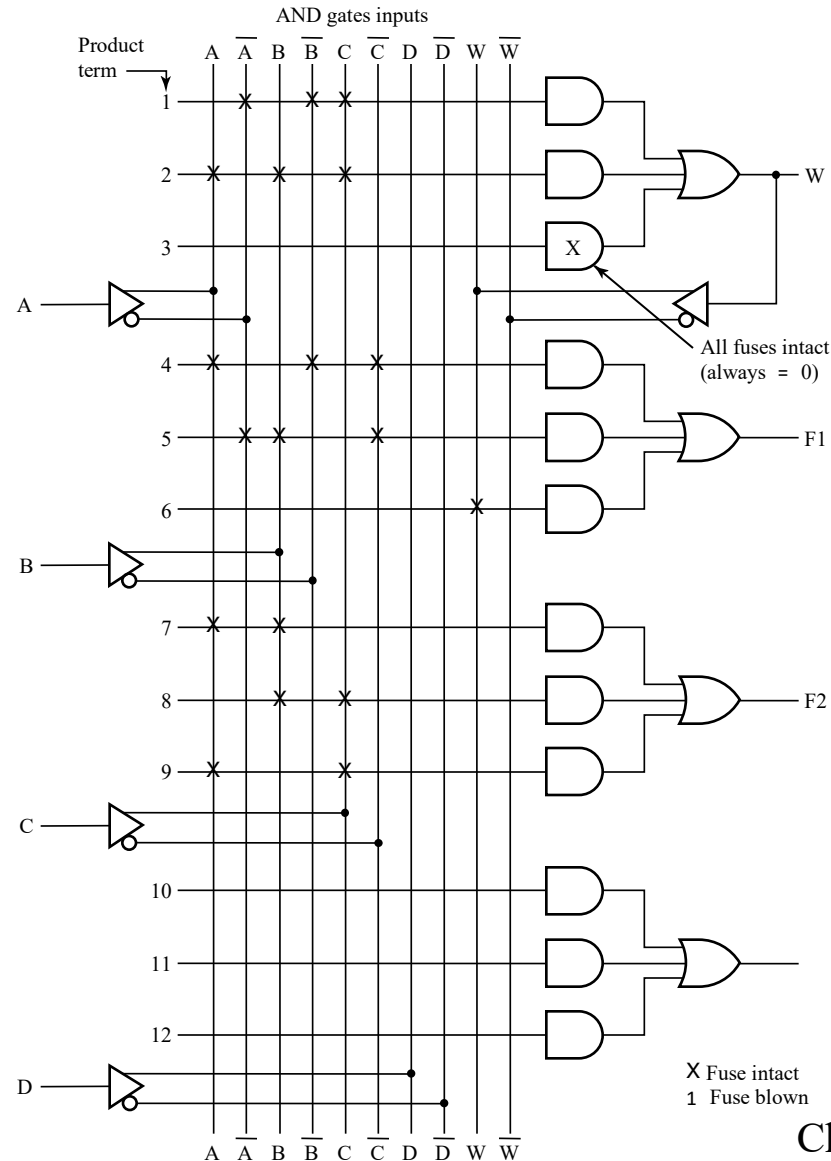

Programmable Logic Array (PLA)


- Compared to a ROM and a PAL, a PLA is the most flexible having a programmable set of ANDs combined with a programmable set of ORs.
- Advantages
 - A PLA can have large N and M permitting implementation of equations that are impractical for a ROM (because of the number of inputs, N, required)
 - A PLA has all of its product terms connectable to all outputs, overcoming the problem of the limited inputs to the PAL Ors
 - Some PLAs have outputs that can be complemented, adding POS functions

Programmable Logic Array (PLA)

■ Disadvantages

- Often, the product term count limits the application of a PLA.
- Two-level multiple-output optimization is required to reduce the number of product terms in an implementation, helping to fit it into a PLA.
- Multi-level circuit capability available in PAL not available in PLA. PLA requires external connections to do multi-level circuits.

Programmable Logic Array Example

 

■ What are the equations for F_1 and F_2 ?

■ Could the PLA implement the functions without the XOR gates?


- 3-input, 2-output PLA with 4 product terms

Programmable Logic Array

- The set of functions to be implemented must fit the available number of product terms
- The number of literals per term is less important in fitting
- The best approach to fitting is multiple-output, two-level optimization (which has not been discussed)
- Since output inversion is available, terms can implement either a function or its complement
- For small circuits, K-maps can be used to visualize product term sharing and use of complements
- For larger circuits, software is used to do the optimization including use of complemented functions

Programmable Logic Array Example

 - K-map specification
- How can this be implemented with four terms?



- Complete the programming table

$$F_1 = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C}$$

$$\bar{F}_1 = AB + AC + BC + \bar{A}\bar{B}\bar{C}$$


$$F_2 = AB + AC + BC$$

$$\bar{F}_2 = \bar{A}\bar{C} + \bar{A}\bar{B} + \bar{B}\bar{C}$$

PLA programming table

				Outputs		
	Product term	Inputs			(C)	(T)
		A	B	C	F_1	F_2
AB	1	1	1	–	1	1
AC	2	1	–	1	1	1
BC	3	–	1	1	1	1
$\bar{A}\bar{B}\bar{C}$	4	0	0	0	1	–

Programmable Logic Array Example

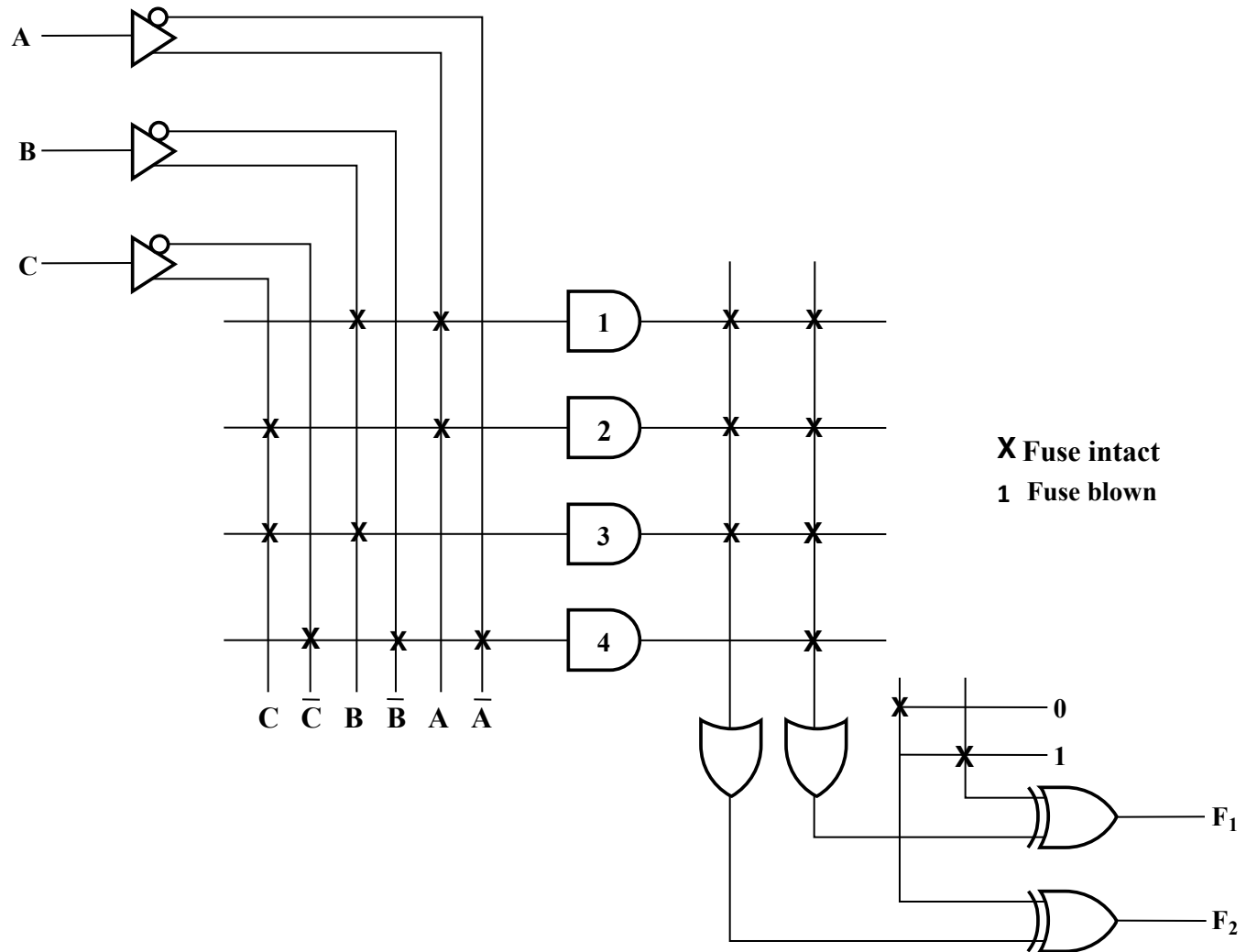

Assignments

- 5-3, 5-4, 5-12