

数逻

好乱的笔记，不建议看...还缺斤少两的

0.1 assessment


- Theory: 70%
 - Quizzes $40\% * 70\% = 28\%$
 - Projects: $20\% * 70 = 14\%$
 - *The final Examination: $40\% * 70\% = 28\%$*
- Necessary condition: the score ≥ 50
Experiments: 30%
- Quizzes
 - Not regular and without notification (once every 2-3 weeks)
 - Questions are from textbook and home assignments
- **Project:**
 - **The source code, source project and technical report should be submitted**
 - **The technical report: including the analysis and design process, the debugging process, and the simulation sequential diagram**
 - **Deadline: One week after the final examination**
- English / Chinese

Requirements of Experiments

- Study Verilog HDL language by yourself
- In advance of each experiment related to Verilog HDL, every one should input and debug the Verilog source code and perform the behavior simulation

1 digital systems and information

1.1 digital system and computers

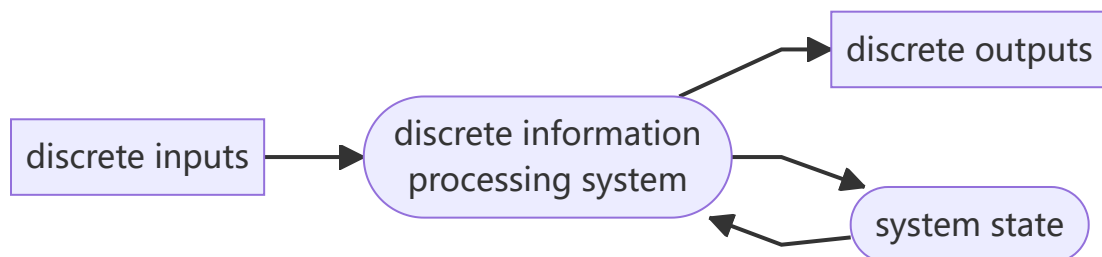

types of digital systems:

- Combinational Logic System
 - No state present
 - $\text{Output} = \text{Function}(\text{Input})$

- Sequential System
 - State present
 - State updated at discrete times
 => **Synchronous** Sequential System
 (同步的，正确度，离散的|固定时间变化的)
 - State updated at any time
 => **Asynchronous** Sequential System
 (异步的，效率，即时变化的)
 - State = Function (State, Input)
 - Output = Function (State) or Function (State, Input)

1.2 information representation

signal example – physical quantity

1.3 number system(binary, octal, hexadecimal)

positional number system(binary for example):

radix(base): $r = 2$

digitals: 0, 1

radix point

weight: $W_i = 2^i$

1.4 coding – decimal code

- By the binary number system, binary numbers can represent decimal numbers. However,
- Computers input and output data used by most people need to be in the decimal system. Working in the manner of the decimal system is highly important.

1.4.1 decimal codes – binary coded decimal(BCD)

Decimal	8,4,2,1	Excess 3	8,4,-2,-1	Gray
0	0000	0011	0000	0000
1	0001	0100	0111	0100
2	0010	0101	0110	0101
3	0011	0110	0101	0111
4	0100	0111	0100	0110
5	0101	1000	1011	0010
6	0110	1001	1010	0011
7	0111	1010	1001	0001
8	1000	1011	1000	1001
9	1001	1100	1111	1000

redundancy 冗余码

(in the form of extra bits, can be incorporated into

binary code words to detect and correct errors.) (lg: Parity)

ASCII (American Standard Code for Information Interchange):
0 ~ 9 : $30_{16} \sim 39_{16}$
Upper case A ~ Z : $41_{16} \sim 5A_{16}$
Lower case a ~ z : $61_{16} \sim 7A_{16}$

2 combinational logic circuits

实实在在的电路——做不做得出来、成本面积速度

logical operations: AND OR NOT

truth tables

logic gates: relays(继电器)—vacuum tubes(真空管)—transistors(晶体管)

gate delay: the output change does not occur instantaneously

NAND: logically complete

AOI: AND-OR-INVERT

boolean equations(布尔代数式): $\lg A(BC') + D$

(Truth tables are unique; expressions and logic diagrams are not. This gives flexibility in implementing functions.)

order: $() > \text{NOT} > \text{AND} > \text{OR}$ $X + YZ = (X + Y)(X + Z)$

1. $X + 0 = X$	2. $X \cdot 1 = X$	1-4 Existence of 0 and 1
3. $X + 1 = 1$	4. $X \cdot 0 = 0$	
5. $X + X = X$	6. $X \cdot X = X$	5-6 Idempotence
7. $X + \overline{X} = 1$	8. $X \cdot \overline{X} = 0$	7-8 Existence of complement
9. $\overline{\overline{X}} = X$		9 Involution
10. $X + Y = Y + X$	11. $XY = YX$	Commutative
12. $(X + Y) + Z = X + (Y + Z)$	13. $(XY)Z = X(YZ)$	Associative
14. $X(Y + Z) = XY + XZ$	15. $X + YZ = (X + Y)(X + Z)$	Distributive
16. $\overline{X + Y} = \overline{X} \cdot \overline{Y}$	17. $\overline{X \cdot Y} = \overline{X} + \overline{Y}$	DeMorgan's

- $x \cdot y + \bar{x} \cdot y = y$ $(x + y)(\bar{x} + y) = y$ **Minimization**
- $x + x \cdot y = x$ $x \cdot (x + y) = x$ **Absorption**
- $x + \bar{x} \cdot y = x + y$ $x \cdot (\bar{x} + y) = x \cdot y$ **Simplification**
- $x \cdot y + \bar{x} \cdot z + y \cdot z = x \cdot y + \bar{x} \cdot z$ **Consensus**
 $(x + y) \cdot (\bar{x} + z) \cdot (y + z) = (x + y) \cdot (\bar{x} + z)$
- $\overline{x + y} = \bar{x} \cdot \bar{y}$ $\overline{x \cdot y} = \bar{x} + \bar{y}$ **DeMorgan's Laws**

The **dual**(对偶) of an algebraic expression is obtained by interchanging $+$ and \cdot , and replacing 0s by 1s and 1 by 0.

self-dual(自对偶) $H = AB + BC + AC$

complementing functions(反函数)

- difference: 对偶-变量不取反

2.0.2 [canonical forms]: SOM/POM

sum of minterms(SOM):

minterms: $XYZ(m_7)$, $XYZ'(m_6)$, $X'Y'Z'(m_0)$... 下标使组合为1

$$f = m_3 + m_2 + m_0 = \sum_m(0, 2, 3)$$

product of maxterms(POM):

maxterms: $X+Y+Z(M_0)$, $X+Y+Z'(M_1)$, $X'+Y'+Z'(M_7)$... 下标使组合为0

$$f = M_2 \cdot M_3 = \Pi_M(2, 3)$$

$$M_i = m_i', \quad m_i = M_i'$$

We can implement any function by "**ORing**" the **minterms** corresponding to "**1**" entries in the function table. These are called the minterms of the minterms of the function. ("ANDing", maxterms, "0")

$$F(x, y, z) = \sum_m(1, 3, 5, 7) :$$

$$F'(x, y, z) = \sum_m(0, 2, 4, 6) = \Pi_M(1, 3, 5, 7)$$

2.0.3 [standard forms]: SOP/POS

standard sum of products(SOP): $F = Y' + X'YZ' + XY$

standard product of sums(POS): $F = X(Y' + Z)(X + Y + Z')$

2.0.4 other gate types:

Buffer ($F = X$)

the 3-StateBuffer (when $EN = 0$, whatever IN is, $OUT = Hi-Z$)

Transmission Gate (can be regarded as a switch)

Hi-Z: 数字电路常见术语, 指的是电路的一种输出状态, 既不是高电平也不是低电平, 如果高阻态再输入下一级电路的话, 对下级电路无任何影响, 和没接一样, 如果用万用表测的话有可能是高电平也有可能是低电平, 随它后面接的东西定。

2.0.5 circuit optimization:

cost criteria (成本标准):

- Literal cost (L)
- Gate input cost (G)
- Gate input cost with NOTs (GN)

2.0.6 boolean function optimization:

Karnaugh Maps (K-map), dimension of squares

2.0.7 Systematic Simplification:

Prime Implicant (质蕴含项)

Essential Prime Implicant(基本质蕴含项)

3 Combinational Logic Design

3.1 implementation technology and logic

combinational circuits(组合电路):

m Boolean inputs, n Boolean outputs, and n switching functions, each mapping the 2^m input combinations to an output such that the current output depends only on the current input values

Technology Parameters(工艺参数):

- Fan-in – the number of inputs available on a gate
- Fan-out – the number of standard loads driven by a gate output
- Logic Levels – the signal value ranges for 1 and 0 on the inputs and 1 and 0 on the outputs (see Figure 1-1)
- Noise Margin – the maximum external noise voltage superimposed on a normal input value that will not cause an undesirable change in the circuit output
- Cost for a gate - a measure of the contribution by the gate to the cost of the integrated circuit
- Propagation Delay(传输延迟) – The time required for a change in the value of a signal to propagate from an input to an output
 - transport delay(输送延迟)
 - inertial delay(惯性延迟):rejection time
- Power Dissipation – the amount of power drawn from the power supply and consumed by the gate

Design procedure:

specification-formulation-optimization-technology mapping-verification

beginning hierarchical(分层的) design

Top-down, Bottom-up

mapping to NAND / NOR gates

3.2 combinational logic:

function block

Rudimentary (基本的) logic functions

Enabling function (使能)

Decoding and decoder (解码器) generate Minterms

lg: two 1-to-2-Line Decoders and four AND gates can generate one 2-to-4-Line Decoder

n-to-2ⁿ-Line Decoder: even $2 \times 2^{k/2}$ odd $2^{(k+1)/2} + 2^{(k-1)/2}$

Encoding and encoder (编码器)

Multiplexer (选择器)

We will refer to the combination of AND gates and OR gates as an $m \times 2$ AND-OR, where m is the number of AND gates and 2 is the number of inputs to the AND gates.

3.3 Arithmetic Functions

3.3.1 Iterative combinational circuits

- Arithmetic functions
 - Operate on binary vectors
 - Use the same subfunction in each bit position
- Can design functional block for subfunction and repeat to obtain functional block for overall function
- *Cell* - subfunction block
- Iterative array - an array of interconnected cells
- An iterative array can be in a single dimension (1D) or multiple dimensions

3.3.2 Binary adders

3.3.2.1 Half-Adder

a half adder adds two bits to produce a two-bit sum (a sum bit S and a carry bit C)

$$S = X \oplus Y = XY' + X'Y = (X+Y) (X'+Y')$$

$$C = XY$$

3.3.2.2 Full-Adder

includes a carry-in bit from lower stages

$$S = X \oplus Y \oplus Z = XY'Z' + X'YZ' + X'Y'Z + XYZ$$

$$C = XY + XZ + YZ = XY + (X \oplus Y)Z$$

3.3.2.3 Ripple Carry Adder (纹波进位加法器)

a n-bit Ripple Carry Adder made from n 1-bit Full Adders

One problem with the addition of binary numbers is the length of **time** to **propagate** the ripple carry from the least significant bit to the most significant bit.

3.3.2.4 Carry-Look-Ahead Adder (超前进位加法器)

G_i (generate): $A_i B_i$

P_i (propagate): $A_i \oplus B_i$

$S_i = P_i \oplus C_i$

$C_{i+1} = G_i + P_i C_i$

C_i can be removed from the cells and used to derive a set of carry equations spanning multiple cells

This could be extended to more than four bits, but in practice, due to limited gate fan-in, such extension is not feasible.

Solution:

$G_{0-3} = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0$

$P_{0-3} = P_3 P_2 P_1 P_0$

$C_4 = G_{0-3} + P_{0-3} C_0$

3.3.3 Binary subtraction

- Subtract the subtrahend N from the minuend M
- If no end borrow occurs, then $M \geq N$, and the result is a non-negative number and correct.
- If an end borrow occurs, then $N > M$ and the difference $M - N + 2^n$ is subtracted from 2^n , and a minus sign is appended to the result.
- The subtraction, $2^n - N$, is taking the 2's complement of N

3.3.3.1 Complements

Diminished Radix Complement of N:

$(r - 1)$'s complement for radix r, define as $(r^n - 1) - N$

Radix Complement:

r's complement for radix r: $r^n - N$

3.3.3.2 Subtraction with 2's complement

For n-digit, unsigned numbers M and N, find $M - N$ in base 2:

- Add the 2's complement of the subtrahend N to the minuend M:
 $M + (2^n - N) = M - N + 2^n$
- If $M > N$, the sum produces end carry 2^n which is discarded; from above, $M - N$ remains.

- If $M < N$, the sum does not produce an end carry and, from above, is equal to $2^n - (N - M)$, the 2's complement of $(N - M)$.
- To obtain the result $-(N - M)$, take the 2's complement of the sum and place a - to its left.

3.3.4 Binary adder-subtractors

signed integers representations: signed-magnitude, signed-complement

overflow detection: $V = C_n \oplus C_{n-1}$

3.3.5 Binary multiplication

3.3.6 Other arithmetic functions

convenient to design the functional blocks by *contraction* (收缩) — removal

of redundancy from circuit to which input fixing has been applied

functions:

- incrementing
- decrementing
- multiplication by constant
- division by constant
- zero fill and extension

4 Sequential Circuits

4.1 Storage Elements and Sequential Circuit Analysis

4.1.1 A Sequential circuit contains:

- Storage elements: Latches (锁存器) or Flip-Flops (触发器)
- Combinational Logic


4.1.2 Types of sequential circuits:

- depends on the times at which: storage elements observe their inputs and change their state
- **Synchronous** (同步的) : Behavior defined from knowledge of its signals at discrete instances of time; Storage elements observe inputs and can change state only in relation to a timing signal (clock pulses from a clock)
- **Asynchronous** (异步的) : Behavior defined from knowledge of inputs at any instant of time and the order in continuous time in which inputs change; If clock just regarded as another input, all circuits are asynchronous!; Nevertheless, the synchronous abstraction makes complex designs tractable!


Discrete event simulation (离散事件模拟/仿真)

 4.1.3 Latches (锁存器)


Basic $\bar{S} - \bar{R}$ Latch : two NAND gates



Basic $S - R$ Latch: two NOR gates

 


 Clock $S - R$ Latch: adding two NAND to the Basic $\bar{S} - \bar{R}$ Latch



C	S	R	Q(t+1)
0	X	X	No Change
1	0	0	No Change
1	0	1	0: Clear Q
1	1	0	1: Set Q
1	1	1	Indeterminate

 D Latch : adding an inverter to the S-R Latch (No 'indeterminate' states)



D锁存器的缺点：存在空翻现象——如果D锁存器直接用在时序电路中作为状态存储元件，当使能控制信号有效时，会导致该元件内部的状态值随时多次改变，而不是保持所需的原始状态值

解决办法：用两个锁存器，主锁存器在脉冲控制下接收输入数据，从锁存器在脉冲结束后改变并保持状态。

4.1.4 Flipflop (触发器)


S - R Master - Slave Flip - Flop :

在有脉冲（高电平）时，修改第一个锁存器的值，保持第二个锁存器的值；在没有脉冲（低电平）时候保持第一个锁存器的值，修改第二个锁存器的值，更新触发器的状态。

The input is observed by the first latch with $C = 1$

The output is changed by the second latch with $C = 0$

 (Problem: delay, S/R are permitted to change while $C = 1$)



Edge - Triggered D Flip - Flop :


仅在时钟的边缘触发，即在特定时刻仅接受一个输入。

（正边沿）关注上升沿前后，上升沿前一刻，主锁存器可写，从锁存器只读；上升沿后一刻，主锁存器只读，从锁存器只写，且写入的是主锁存器存储的值——换句话说，存的是上升沿前一刻写入主锁存器的内容。


The delay of the S-R master-slave flip-flop can be avoided since the 1s-catching behavior is not present with D replacing S and R inputs.

The change of the D flip-flop output is associated with the negative edge at the end of the pulse.

 (also called a *negative-edge triggered flip-flop*)




 *standard flip-flop (Positive-Edge Triggered D Flip-Flop) * not actual used one*




STANDARD SYMBOLS:

Standard Symbols for Storage Elements

 


■ Master-Slave:

Postponed output indicators

 

■ Edge-Triggered:

Dynamic indicator

 

4.1.5 Direct inputs:

At power up or at reset, all or part of a sequential circuit usually is initialized to a known state before it begins operation.

This initialization is often done outside of the clocked behavior of the circuit.

direct R and S inputs that control the state of the latches within the flip-flops are used for this initialization.

(S=1,Q=1;R=1,Q=0)

4.1.6 Sequential Circuit Analysis

General Model:

output = Boolean function of state (and input).

state = Boolean function of **last** state and input.


State Table:

present state, input, next state, output

(当前状态的分析 and 定义有很多不同情况)

State Diagrams:

 - A *circle* with the *state name* in it for each state
- A *directed arc* from the Present State to the Next State for each *state transition*
- A *label* on each directed arc with the *Input values* which causes the state transition, and a label on each circle with the *output value* produced, or on each directed arc with the output value produced.




Equivalent State Definitions:

Two states are equivalent if their response for each possible **input** sequence is an identical output sequence.


Alternatively, two states are equivalent if their **outputs** produced for each input symbol is identical and their **next states** for each input symbol are the same or equivalent.

Finite State Machines (FSMs) : Sequential Circuits or Sequential Machines

 Moore Model Diagrams: maps states to outputs



 Mealy Model Diagrams: maps inputs and state to outputs



Mixed Moore and Mealy Outputs

4.1.7 Flip-Flop Parameters (参数)

t	mean
t_s	setup time
t_h	hold time
t_w	clock pulse width
t_{px}	propagation delay
t_{pd}	$\max(t_{pHL}, t_{pLH})$

Flip-Flop Timing Parameters

■ t_s - setup time

■ t_h - hold time


■ t_w - clock pulse width

■ t_{px} - propagation delay


• t_{PHL} - High-to-Low

• t_{PLH} - Low-to-High

• $t_{pd} - \max(t_{PHL}, t_{PLH})$

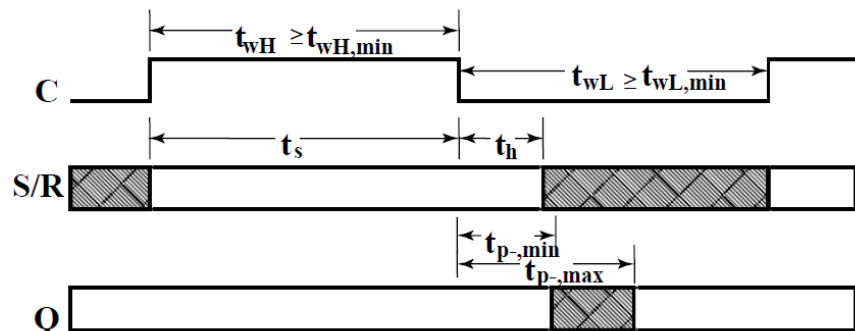

(a) Pulse-triggered (positive pulse)

 

(b) Edge-triggered (negative edge)

4.1.8 Circuit and System Level Timing

$t_p = t_{stack} + (t_{pd,FF} + t_{pd,COMB} + t_s)$, t_{stack} is greater than or equal to zero

4.2 Sequential Circuit Design

4.2.1 The Design Procedure

- Specification
- Formulation - Obtain a state diagram or state table
- State Assignment - Assign binary codes to the states
- Flip-Flop Input Equation Determination - Select flip-flop types and derive flip-flop equation from the next state entries in the table
- Output Equation Determination - Derive output equations from output entries in the table
- Optimization - Optimize the equations
- Technology Mapping - Find circuit from equations and map to flip-flop and gate technology
- Verification - Verify correctness of final design

4.2.2 Sequence Recognizer Procedure

- Begin in an **initial state** in which NONE of the initial portion of the sequence has occurred (typically “reset” state).
- Add a state that recognizes that the first symbol has occurred.
- Add states that recognize each successive symbol occurring.
- The final state represents the **input sequence** (possibly less the final input value) occurrence.
- Add state transition arcs which specify what happens when a symbol **not** in the proper sequence has occurred.
- Add other arcs on non-sequence inputs which transition to states that represent the input subsequence that has occurred.

4.2.3 Formulation: Find State Table

Present State	Next State		Output
	x=0	x=1	
A	A	B	0 0
B
C

Mealy Model

Present State	Next State		Output
	x=0	x=1	
A	A	B	0
B
C

Moore Model

Mealy Model侧重记录输入前的状态；Moore Model侧重输入后的状态

Moore is More

4.2.4 状态表的简化

等效状态：设状态S1和S2是完全确定状态表中的两个状态,如果对于所有可能的输入序列，分别从状态S1和状态S2出发，所得到的输出响应序列完全相同，则状态S1和S2是等效的，记作(S1, S2), 或者说，状态S1和S2是等效对。等效状态可以合并。这里“所有可能的输入序列”是指长度和结构是任意的，它包含无穷多位，且有无穷多种组合。

输出相同 & (次态相同 | 次态交错 | 次态循环)

观察法、隐含表法（处于循环链中是等效的;互相依赖的是等效的）

4.2.5 状态分配

任务：决定编码的长度，寻找一种最佳的或接近最佳的状态分配方案

原则：

- 在相同输入条件下具有相同次态的现态，应尽可能分配相邻的二进制代码
- 在相邻输入条件，同一现态的次态应尽可能分配相邻的二进制代码

- 输出完全相同的现态应尽可能分配相邻的二进制代码
- 最小化状态表中出现次数最多的状态或初始状态应分配逻辑0

4.2.6 Other Flip-Flop Types

J-K Flip-flop:

$J = K = 1$ is allowed, and the flip-flop changes to the opposite state

has some “1’s catching” behavior as S-R flip-flop

if the master changes to the wrong state, it will be passed to the slave

T Flip-flop:

$T = 0$, no change to state; $T = 1$, changes to opposite state

J-K flip-flop with $J = K = T$

“1’s catching”

cannot be initialized to a known state using the T input (Reset essential)

4.2.7 Basic Flip-flop Descriptors

Characteristic Table:

D	Q(t+1)	Operation
0	0	Reset
1	1	Set

Characteristic Equation:

$$Q(t+1) = D$$

$$Q(t+1) = T \otimes Q$$

$$Q(t+1) = S + R' Q, S \cdot R = 0$$

$$Q(t+1) = J Q' + K' Q \quad (AB + A' C + BC = AB + A' C)$$

Excitation Table:

Q(t+1)	D	Operation
0	0	Reset
1	1	Set

4.3 State Machine Design

5 Digital Hardware Implementation

5.1 The Design Space

5.2 Programmable Implementation Technologies

- Why Programmable Logic
- Programmable Logic-More Advantages
- Programming Technologies


5.2.1 Programmable Configuration

- **Read Only Memory (ROM):** a fixed array of AND gates and a programmable array of OR gates
- **Programmable Array Logic (PAL):** a programmable array of AND gates feeding a fixed array of OR gates
- **Programmable Logic Array (PLA):** a programmable array of AND gates feeding a programmable array of OR gates
- **Complex Programmable Logic Device (CPLD) / Field-Programmable Gate Array (FPGA):** complex enough to be called “architectures”


ROM, PAL and PLA Configurations



(a) Programmable read-only memory (PROM)

 

 (b) Programmable array logic (PAL) device



(c) Programmable logic array (PLA) device

6 Registers and Register Transfers

6.1 Registers, Microoperations and Implementations

Register: a collection of binary storage elements

Register Design Models:

- Add predefined combinational circuits to registers
- Design individual cells using the state diagram / state table model and combine them into a register (Output is usually the state variable)

Register Storage and Load Enable: Load = 1, load the values on the data inputs; Load = 0, store the values in the register.

- **Registers with Clock Gating:** the \overline{Load} signal enables the clock signal to pass through if 0 and prevents the clock signal from passing through if 1. $Gated\ Clock = Clock + \overline{Load}$.
Problem: Clock Skew of gated clocks with respect to clock or each other

- **Registers with Load-Controlled Feedback:** Run the clock continuously, and selectively use a load control to change the register contents.
(Example) 2-bit register: Load = 0, loads register contents; = 1, input values.

Register Transfer Operations:

the movement and processing of data stored in registers

three basic components: set of registers, operations, control of operations

Elementary Operations (Microoperations): load, count, shift, add, bitwise"OR", etc

Register Notation:

- Letters and numbers – denotes a register (ex. R2, PC, IR)
- Parentheses () – denotes a range of register bits (ex. R1(1), PC(7:0), PC(L))
- Arrow (\leftarrow) – denotes data transfer (ex. $R1 \leftarrow R2$, $PC(L) \leftarrow R0$)
- Comma – separates parallel operations
- Brackets [] – Specifies a memory address (ex. $R0 \leftarrow M[AR]$, $R3 \leftarrow M[PC]$)

Conditional Transfer: If ($K1 = 1$) then ($R2 \leftarrow R1$) is shortened to **K1: ($R2 \leftarrow R1$)**

Control Expressions:

appears to the left of the operation and is separated from it by a colon

specify the logical condition for the operation to occur

(Example) $\overline{X} K1 : R1 \leftarrow R1 + R2$

Microoperations:

- Logical Groupings:
 - Transfer - move data from one register to another
 - Arithmetic - perform arithmetic on data in register (+ - * /)
 - Logic - manipulate data or use bitwise logical operations (\vee \wedge \otimes \neg)
 - Shift - shift data in registers

NOTE:

"+" means "OR" in $K1 + K2$; and means "plus" In $R1 \leftarrow R1 + R3$

Symbolic Designation	Description
$R0 \leftarrow R1 + R2$	Addition
$R0 \leftarrow \overline{R1}$	One's Complement
$R0 \leftarrow \overline{R1} + 1$	Two's Complement
$R0 \leftarrow R2 + \overline{R1} + 1$	R2 minus R1
$R0 \leftarrow R1 + 1$	Increment (count up)
$R0 \leftarrow R1 - 1$	Decrement (count down)


Symbolic Designation	Description
$R0 \leftarrow \overline{R1}$	Bitwise NOT
$R0 \leftarrow R1 \vee R2$	Bitwise OR (set bits)
$R0 \leftarrow R1 \wedge R2$	Bitwise AND (clears bits)
$R0 \leftarrow R1 \otimes R2$	Bitwise EXOR (complements bits)

Symbolic Designation	Description	(R2 = 11001001) R1
$R1 \leftarrow sl\ R2$	Shift Left	10010010
$R1 \leftarrow sr\ R2$	Shift Right	01100100


Register Transfer Structures:

- **Multiplexer-Based Transfers** - Multiple inputs are selected by a multiplexer dedicated to the register

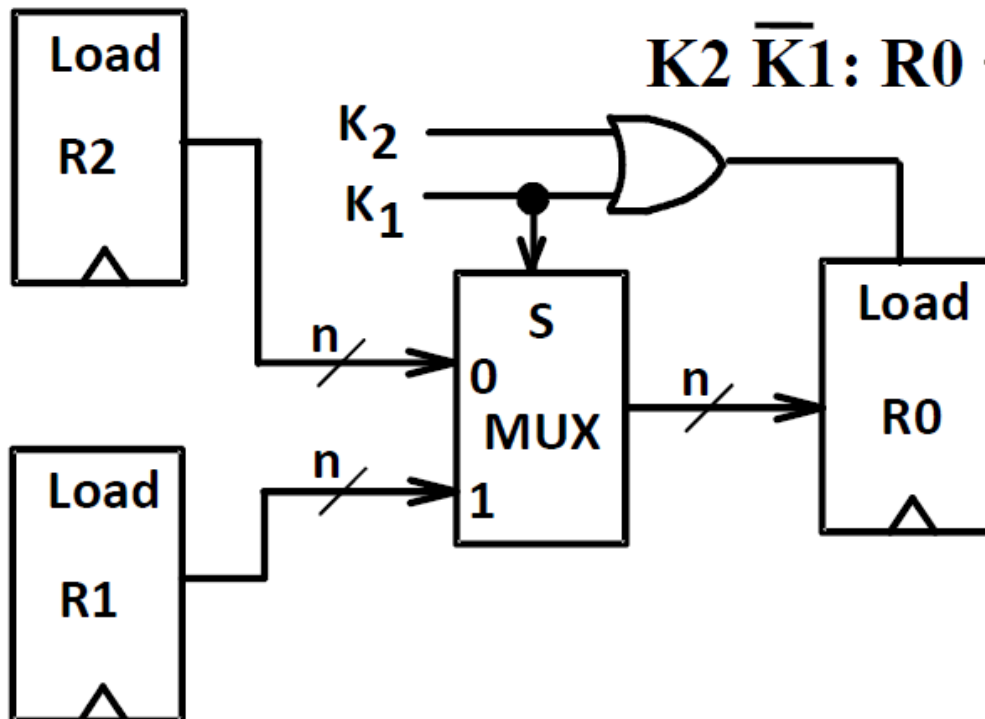The transfers are: **K1: $R0 \leftarrow R1$**
K2 $\overline{K1}$: $R0 \leftarrow R2$



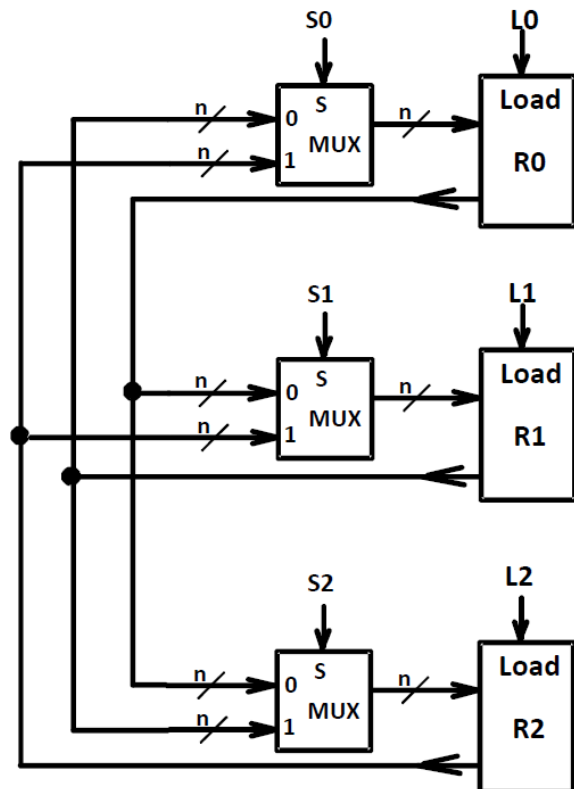
- Multiplexer connected to each register input produces a very flexible transfer structure =>
- Characterize the simultaneous transfers possible with this structure.
- 18 gate inputs per bit plus 3 shared inverters with total of 3 inputs



simultaneous: 同步的


- **Bus-Based Transfers** - Multiple inputs are selected by a shared multiplexer driving a bus that feeds inputs to multiple registers

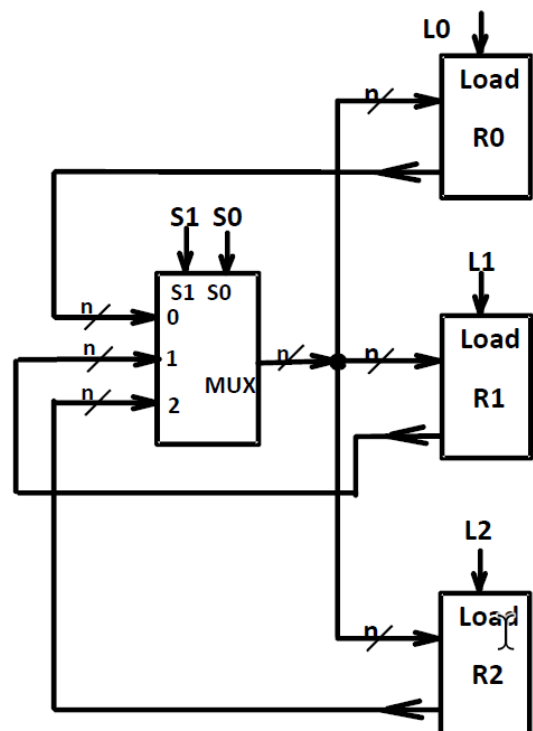- A single bus driven by a multiplexer lowers cost, but limits the available transfers =>
- Characterize the simultaneous transfers possible with this structure.
- Characterize the cost savings compared to dedicated multiplexers
- 9 gate inputs per bit + shared decoder with 8 inputs



- **Three-State Bus** - Multiple inputs are selected by 3-state drivers with outputs connected to a bus that feeds multiple registers

 - **The 3-input MUX can be replaced by a 3-state node (bus) and 3-state buffers.**
- **Cost is further reduced, but transfers are limited**
- **Characterize the simultaneous transfers possible with this structure.**
- **Characterize the cost savings and compare**
- **3 gate inputs per three state driver = 9 gate inputs**
- **Other advantages?**





- **Other Transfer Structures** - Use multiple multiplexers, multiple buses, and combinations of all the above.

Shift Registers:

serial input (串行输入), shift right input (右移输入)

serial output (串行输出), parallel output (并行输出)

  - **A parallel load shift register with an added “hold” operation that stores data:**



LSB是“最低有效位”（Least Significant Bit）的缩写，是指在二进制数中最右边的一位。在计算机科学中，LSB通常用于表示数字的二进制表示中的最后一位。MSB是“最高有效位”（Most Significant Bit）的缩写。

6.2 Counters, Register Cells, Buses, & Serial Operations

Counters: sequential circuits which "count" through a specific state sequence. They can count up, count down, or count through other fixed sequences. Two distinct types are in common usage:


- Ripple Counters (for n bits, total worst case delay is $n t_{\text{PHL}}$)

- Synchronous Counters


- To eliminate the "ripple" effects, use a common clock for each flip-flop and a combinational circuit to generate the next state.

■ Upward Counting Sequence =>

Q_3	Q_2	Q_1	Q_0
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
1	0	1	0
1	0	1	1
1	1	0	0
1	1	0	1
1	1	1	0
1	1	1	1

 

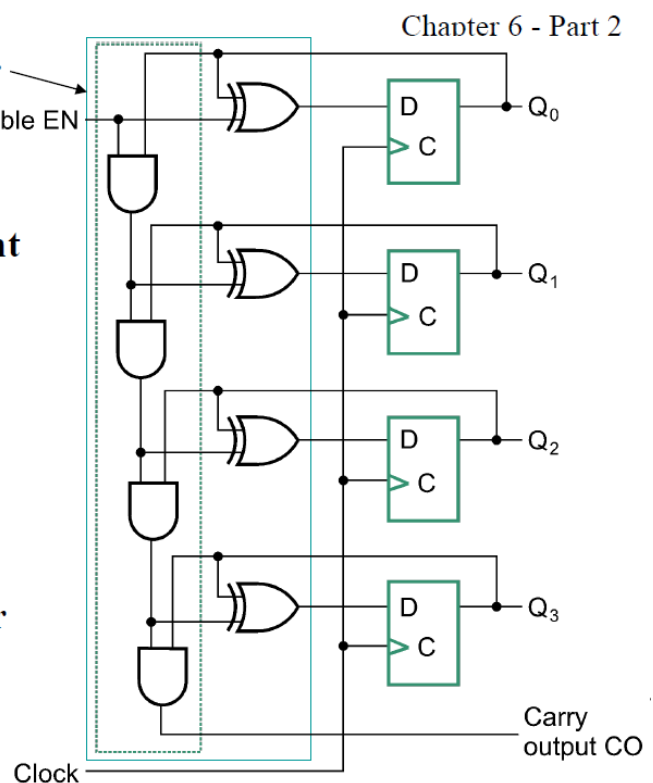- Internal details => Incrementer
- Internal Logic
 - XOR complements each bit
 - AND chain causes complement of a bit if all bits toward LSB from it equal 1
- Count Enable
 - Forces all outputs of AND chain to 0 to "hold" the state
- Carry Out
 - Added as part of incrementer
 - Connect to Count Enable of additional 4-bit counters to form larger counters




(a) Logic Diagram-Serial Gating

■ Carry chain


- series of AND gates through which the carry “ripples”
- Yields long path delays
- Called *serial gating*

■ Replace AND carry chain with ANDs => in parallel

 - Reduces path delays
- Called *parallel gating*
- Like carry lookahead
- Lookahead can be used on COs and ENs to prevent long paths in large counters



(c) Symbol

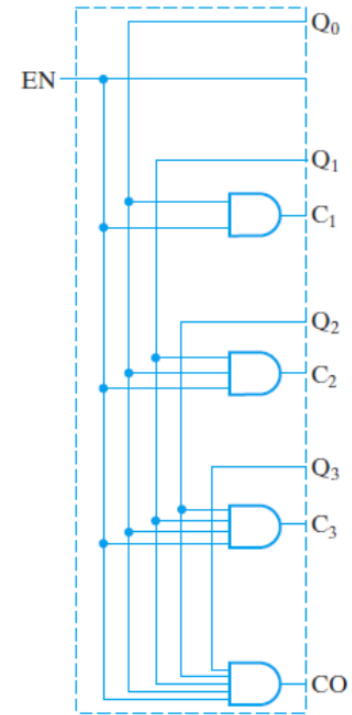

(b) Logic diagram—parallel gating

■ Symbol for Synchronous Counter

• Other Counters

- Down Counter
- Up-Down Counter
- Parallel Load Counter

■ Add path for input data


- enabled for Load = 1

■ Add logic to:

- disable count logic for Load = 1
- disable feedback from outputs for Load = 1
- enable count logic for Load = 0 and Count = 1

■ The resulting function table:

Load	Count	Action
0	0	Hold Stored Value
0	1	Count Up Stored Value
1	X	Load D

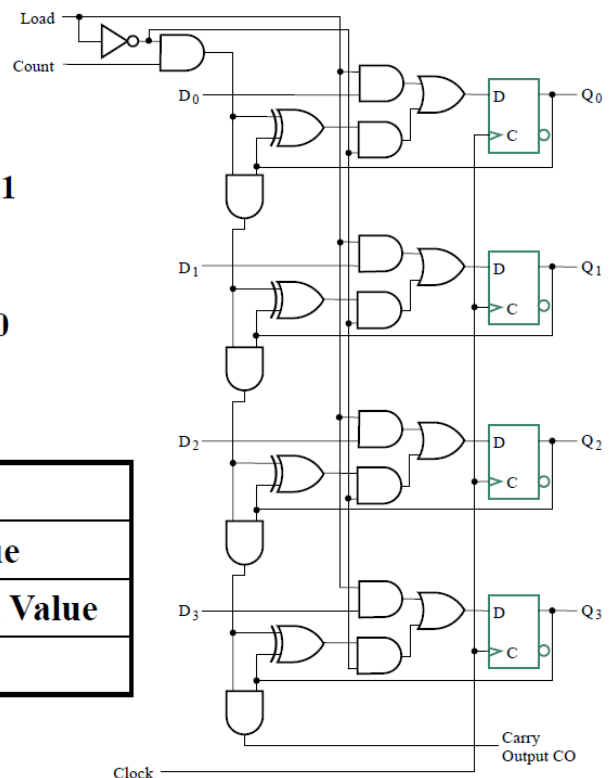

- Divide-by-n Counter


6.3 Control of Register Transfers

7 Memory Basics

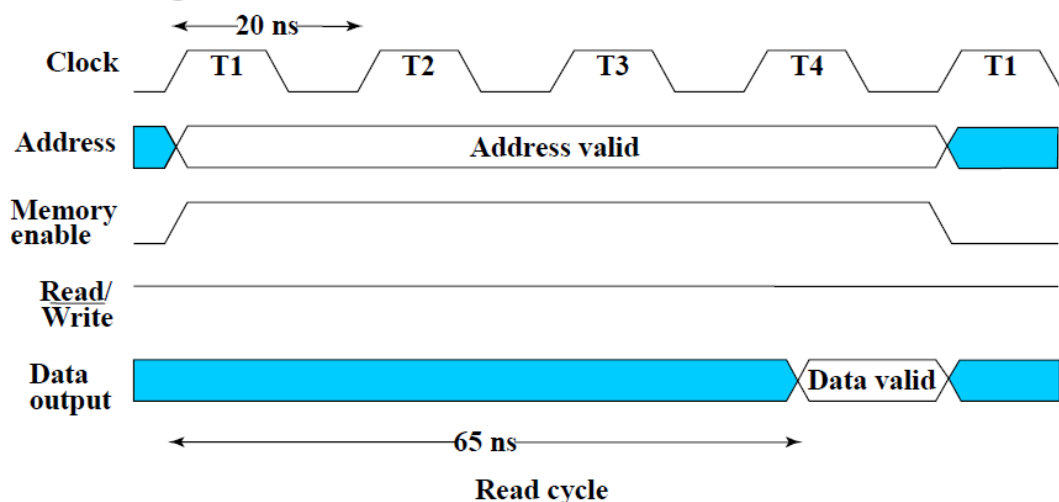
7.1 Memory Definitions

- Memory — A collection of storage cells together with the necessary circuits to transfer information to and from them.
- Memory Organization — the basic architectural structure of a memory in terms of how data is accessed.
- Random Access Memory (RAM) — a memory organized such that data can be transferred to or from any cell (or collection of cells) in a time that is not dependent upon the particular cell selected.
- Memory Address — A vector of bits that identifies a particular memory element (or collection of elements).
- Typical data elements are: bit, byte, word
- Memory Data — a bit or a collection of bits to be stored into or accessed from memory cells.
- Memory Operations — operations on memory data supported by the memory unit. Typically, *read* and *write* operations over some data element (bit, byte, word, etc.).

- **Most basic memories are asynchronous**
 - Storage in latches or storage of electrical charge
 - No clock
- **Controlled by control inputs and address**
- **Timing of signal changes and data observation is critical to the operation**
- **Read timing:**



- Write timing:

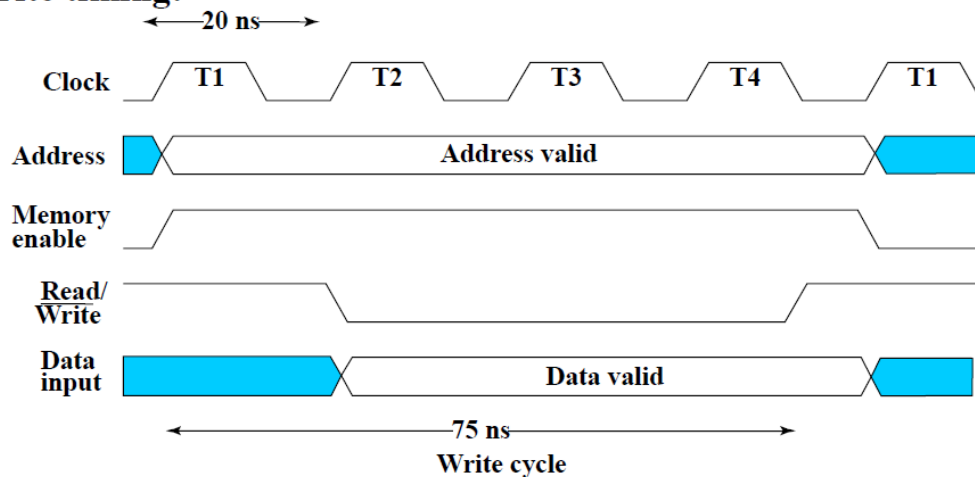

- Critical times measured with respect to edges of write pulse (1-0-1):


- Address must be established at least a specified time before 1-0 and held for at least a specified time after 0-1 to avoid disturbing stored contents of other addresses
- Data must be established at least a specified time before 0-1 and held for at least a specified time after 0-1 to write correctly

7.2 RAM Integrated Circuits

- Types of random access memory:
 - Static: information stored in latches
 - Dynamic: information stored as electrical charges on capacitors
- Dependence on Power Supply
 - Volatile: loses stored information when power turned off
 - Non-volatile: retains information when power turned off

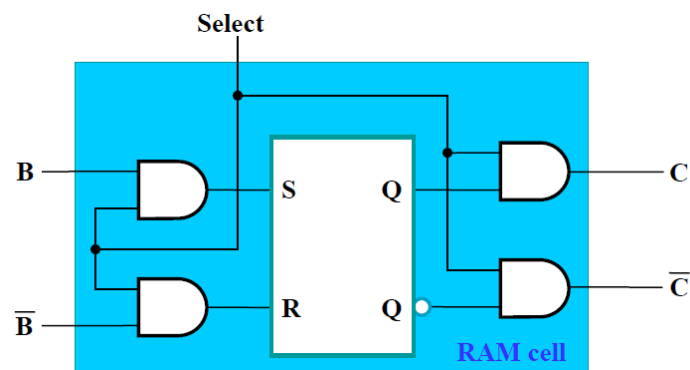7.2.1 Static RAM


Storage cell: SR Latch, Select input for control, Dual Rail Data Input B and B', Dual Rail Data Output C and C'



Static RAM — Bit Slice


- Represents all circuitry that is required for 2^n 1-bit words

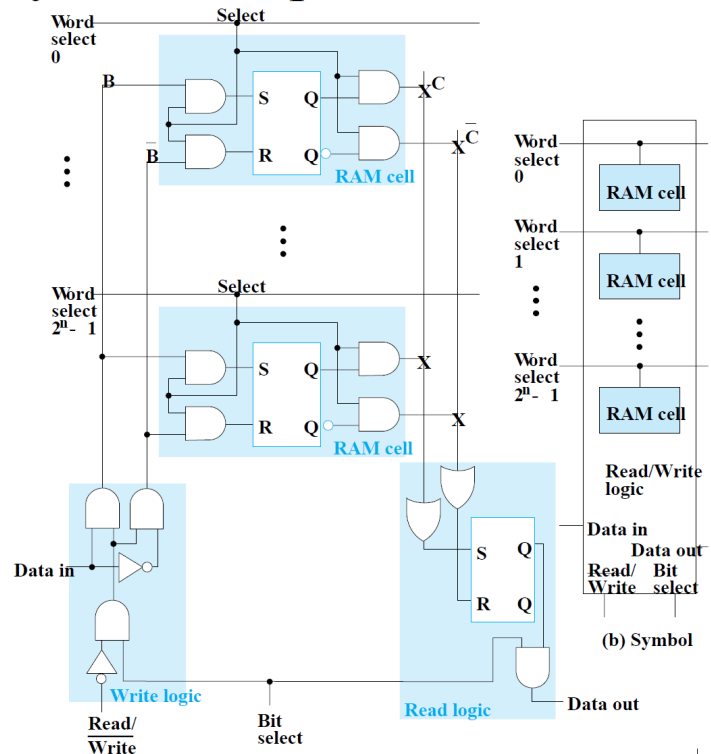
- Multiple RAM cells
- Control Lines:
 - Word select i — one for each word
 - Read / Write
 - Bit Select
- Data Lines:
 - Data in
 - Data out



2^n -Word \times 1-Bit RAM IC

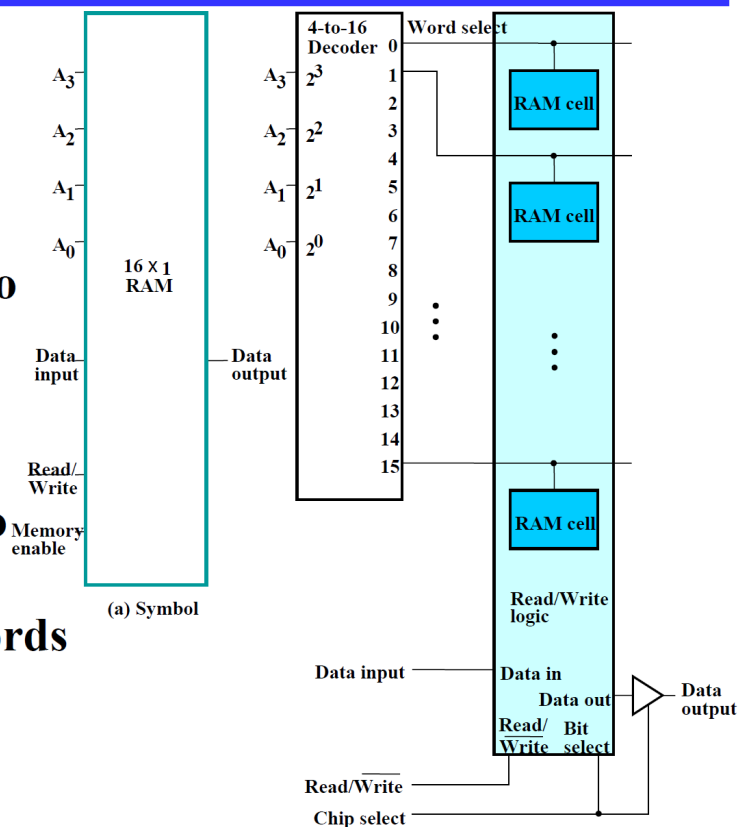- To build a RAM IC from a RAM slice, we need:
 - Decoder — decodes the n address lines to 2^n word select lines
 - A 3-state buffer on the data output permits RAM ICs to be combined into a RAM with $c \times 2^n$ words




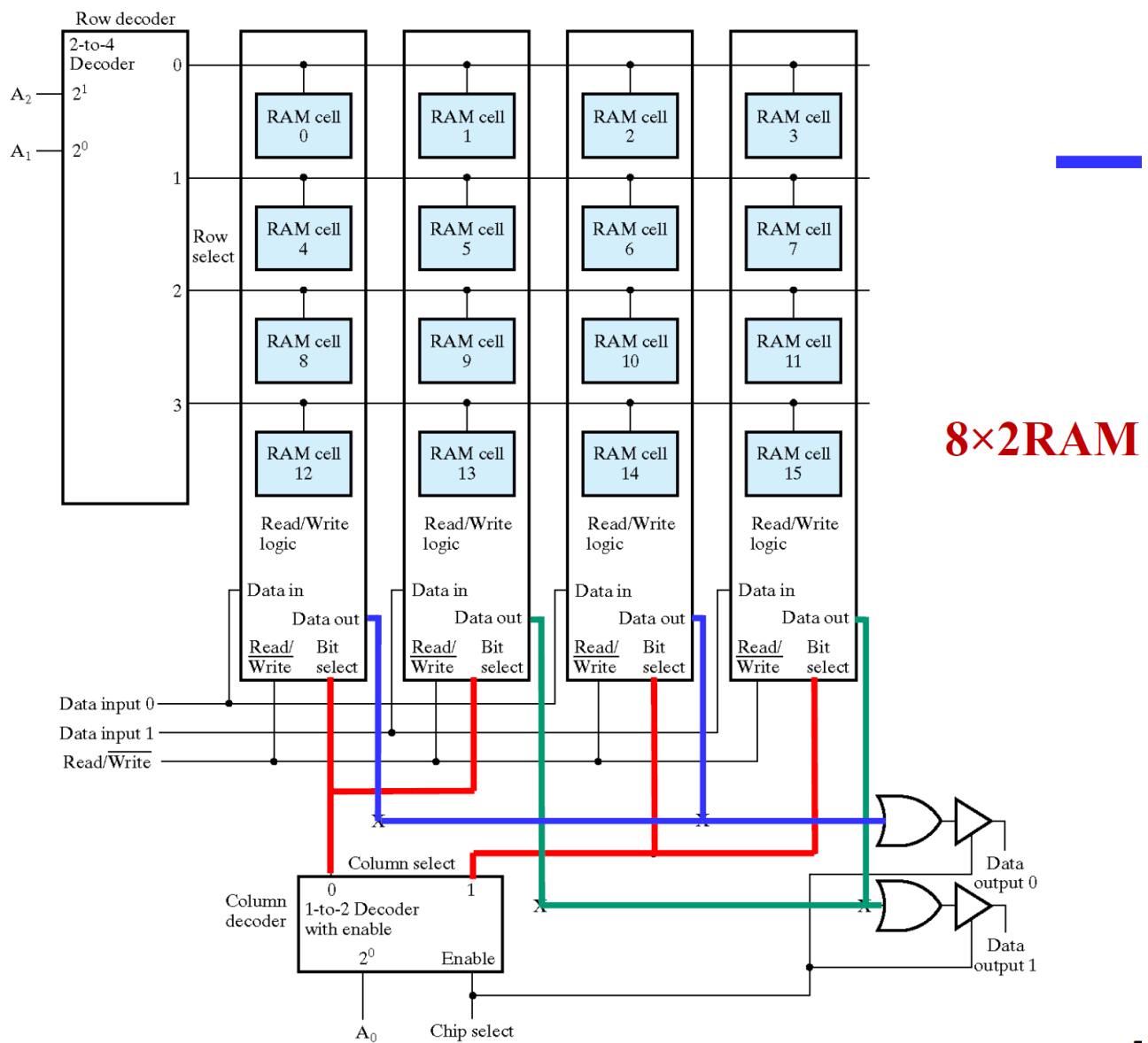

8 x 2 RAM: 8 words, 2 bits


Making Larger Memories

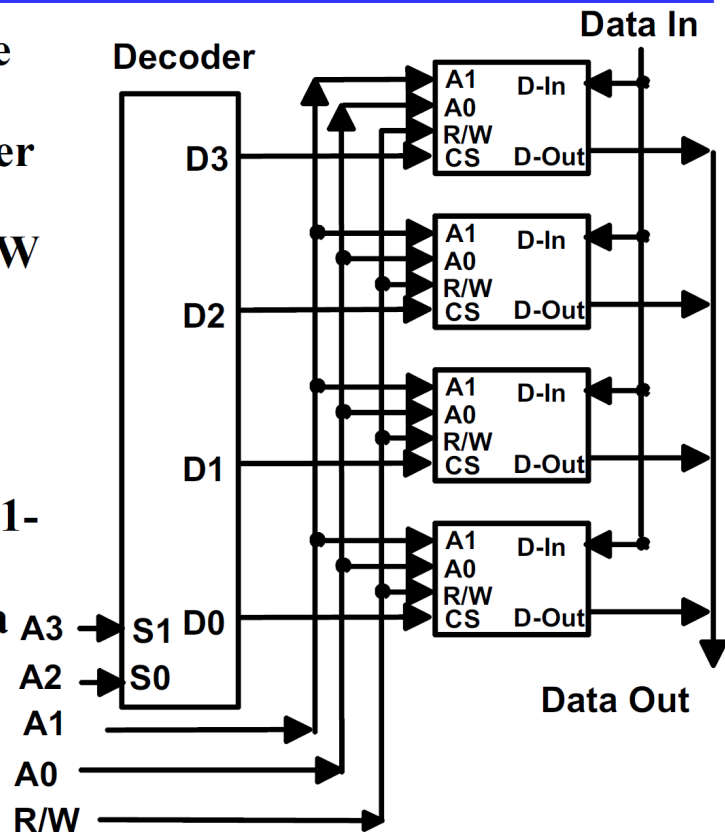- Using the CS lines, we can make larger memories from smaller ones by tying all address, data, and R/W lines in parallel, and using the decoded higher order address bits to control CS.
- Using the 4-Word by 1-Bit memory from before, we construct a 16-Word by 1-Bit memory. \Rightarrow



Making Wider Memories

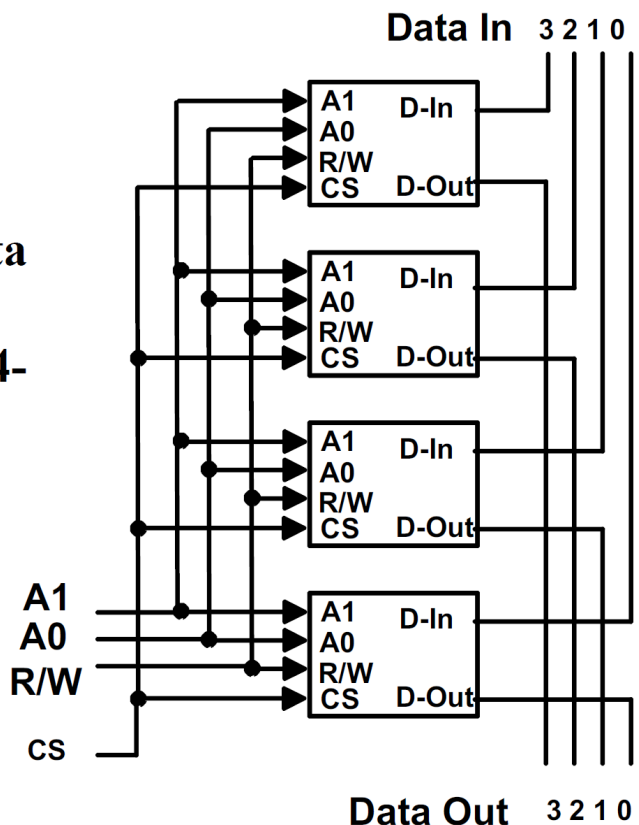- To construct wider memories from narrow ones, we tie the address and control lines in parallel and keep the data lines separate.
- For example, to make a 4-word by 4-bit memory from 4, 4-word by 1-bit memories \Rightarrow
- Note: Both 16x1 and 4x4 memories take 4-chips and hold 16 bits of data.





7.2.2 Dynamic RAM (DRAM)

- Basic Principle: Storage of information on capacitors (电容器)
- Charge and discharge of capacitor to change stored value
- Use of transistor as “switch” to Store charge and Charge or discharge

Dynamic RAM - Bit Slice

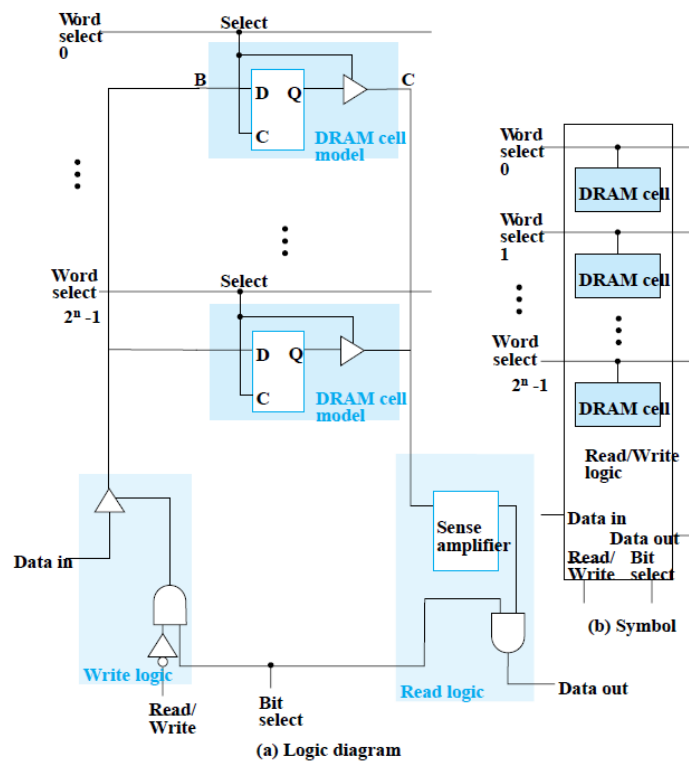- C is driven by 3-state drivers
- Sense amplifier is used to change the small voltage change on C into H or L
- In the electronics, B, C, and the sense amplifier output are connected to make destructive read into non-destructive read



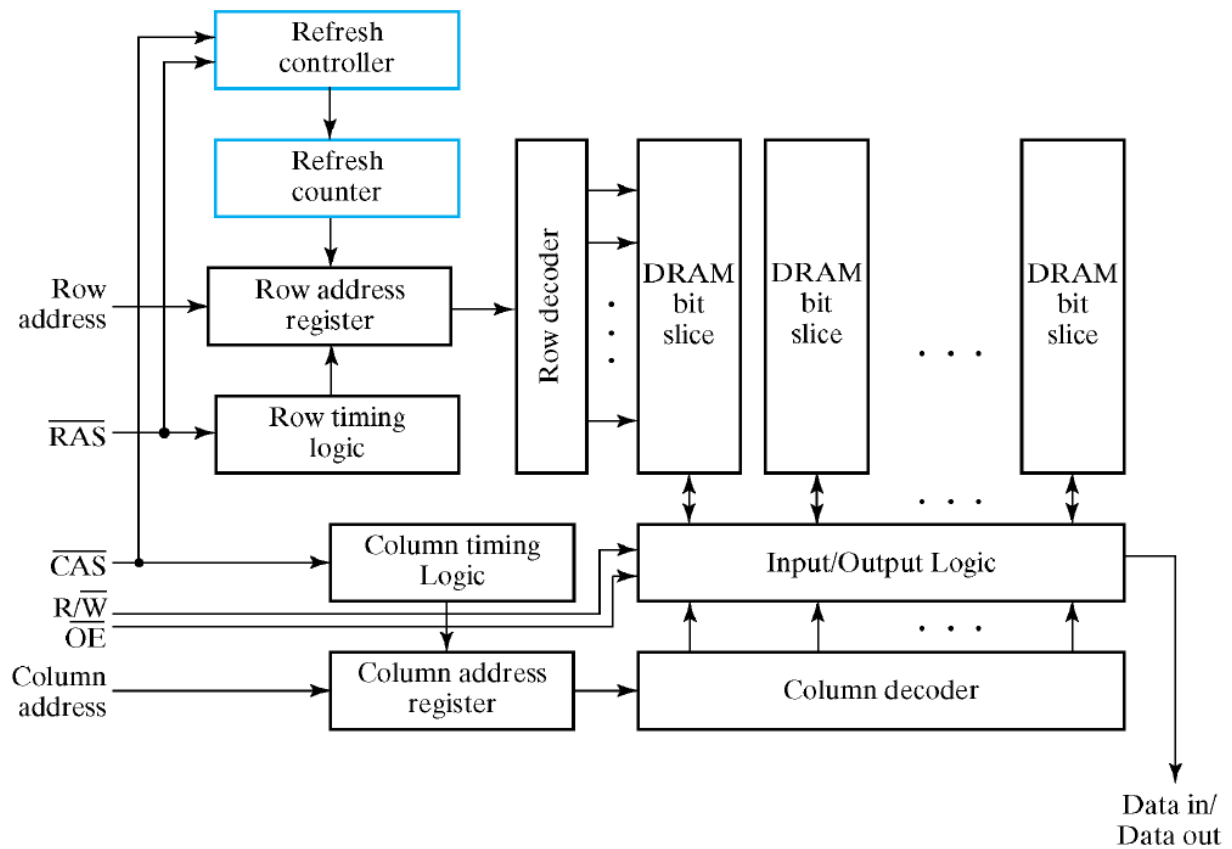

DRAM Types:

- Synchronous DRAM (SDRAM)
- Double Data Rate SDRAM (DDR SDRAM)
- RAMBUS DRAM (RDRAM)